

## **ECE 4643: Power Electronics**

### **Course Project: Part II**

**Due to 2:00 PM, November 8, 2019**

---

Design a DC regulator (Buck-Boost converter) that is supplied from 40 V DC for the following specifications:

1– Output DC voltage varies between 12–90.

2–  $|\Delta v_O| \leq 7\%$  and  $|\Delta i_O| \leq 10\%$ .

3– Load variations:  $0.5 \leq I_O \leq 2.5$  A for which  $V_O$  does not change and  $|\Delta V| \leq \pm 10\%$ .

The designed PEC is to be implemented using MATLAB/SIMULINK