

ECE 4643
POWER ELECTRONICS
LABORATORY : 1

AC-DC Uncontrolled Power Converter

Author 1 :
Riashad Siddique
3674132

Author 2:
Muhammad Naufil Waleed
Khan
3522929

Instructor:
Dr. S. A. Saleh

October 6, 2019



Contents

1	Objective	3
2	1ϕ full wave rectifier	3
2.1	Voltage and Current waveforms	4
2.1.1	200 Ω	4
2.1.2	DC motor	5
2.2	Harmonic Analysis of the waveforms	6
2.2.1	200 Ω	6
2.2.2	DC motor	8
3	3ϕ full wave rectifier	10
3.1	Voltage and Current waveforms	11
3.1.1	200 Ω	11
3.1.2	DC motor	12
3.2	Harmonic Analysis of the waveforms	13
3.2.1	200 Ω	13
3.2.2	DC Motor	15
4	Calculations and Questions	17
5	Discussions and Conclusion	18

List of Figures

1	1 ϕ full wave rectifier	3
2	V_{in} vs I_{in} for 200 Ω	4
3	V_{out} vs I_{out} for 200 Ω	4
4	V_{in} vs I_{in} for DC motor	5
5	V_{out} vs I_{out} for DC motor	5
6	V_{in} Harmonics for 200 Ω	6
7	V_{out} Harmonics for 200 Ω	6
8	I_{in} Harmonics for 200 Ω	7
9	I_{out} Harmonics for 200 Ω	7
10	V_{in} Harmonics for DC motor	8
11	V_{out} Harmonics for DC motor	8
12	I_{in} Harmonics for DC motor	9
13	I_{out} Harmonics for DC motor	9
14	3 ϕ Full wave rectifier	10
15	V_{in} vs I_{in} for 200 Ω	11
16	V_{out} vs I_{out} for 200 Ω	11
17	V_{in} vs I_{in} for DC motor	12
18	V_{out} vs I_{out} for DC motor	12
19	V_{in} Harmonics for 3 ϕ 200 Ω	13
20	V_{out} Harmonics for 3 ϕ 200 Ω	13
21	I_{in} Harmonics for 3 ϕ 200 Ω	14
22	I_{out} Harmonics for 3 ϕ 200 Ω	14
23	V_{in} Harmonics for 3 ϕ DC motor	15
24	V_{out} Harmonics for 3 ϕ DC motor	15
25	I_{in} Harmonics for 3 ϕ DC motor	16
26	I_{out} Harmonics for 3 ϕ DC motor	16

List of Tables

1	Load power factor calculation	17
2	Load efficiency	17
3	Load power loss	17

1 Objective

The objective of this experiment is to investigate the performance of single phase and three phase full wave rectifiers while supplying different load types. We will investigate the input and output harmonics of the AC-DC converter. We will record the efficiency of the system as well as the power factor of the full wave rectifier for the 1ϕ and 3ϕ systems.

2 1ϕ full wave rectifier

The circuit for the 1ϕ full wave rectifier used in the lab is given in the Figure 1. In this experiment the DAM is used to monitor and record the input output voltages and current. The power and reactive power reading is also recorded from the DAM. Different harmonics for both input and output will be observed for both voltages and currents, which is expected due to the diodes involved in the rectification process. The experiment will be first conducted using a $200\ \Omega$ pure resistive load. Later, the resistive will be removed and it will be replaced using a DC motor. In the case of the resistive load the input voltage has to be increased to 60 V from 0 V. While for the DC motor the input voltage is increased to a value of 110 V

For the 1ϕ full wave rectifier, the circuit is setup in the following configuration

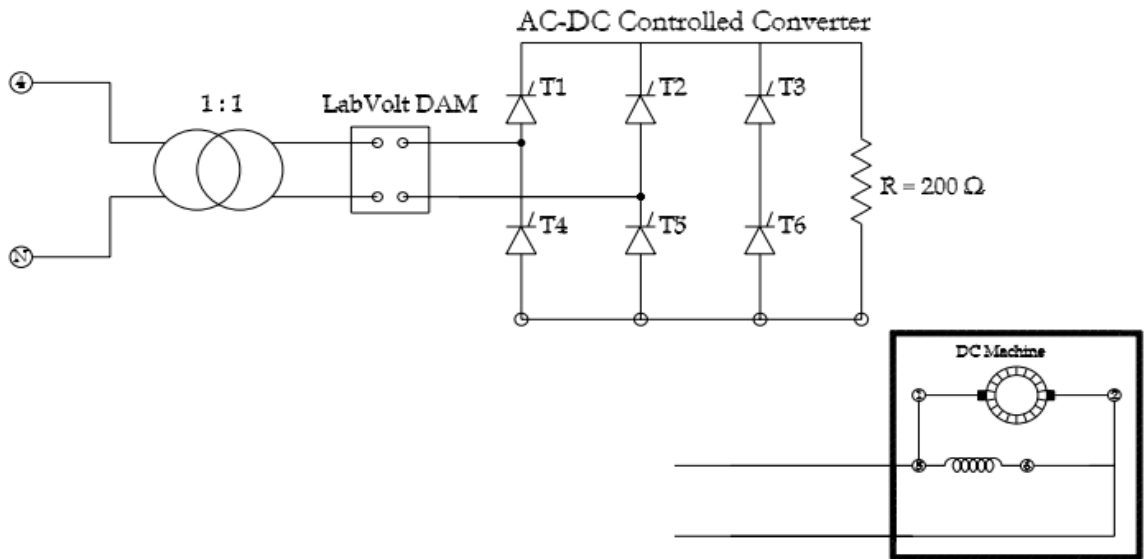


Figure 1: 1ϕ full wave rectifier

2.1 Voltage and Current waveforms

2.1.1 $200\ \Omega$

Input voltage vs the input current waveform for the $200\ \Omega$ is given in the following figure.

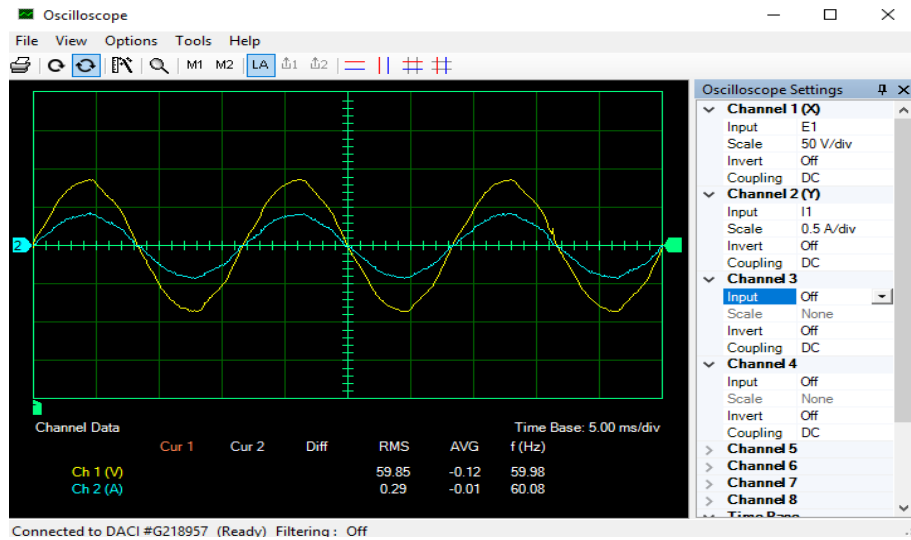


Figure 2: V_{in} vs I_{in} for $200\ \Omega$

Output voltage vs the output current waveform for the $200\ \Omega$ is given in the following figure.

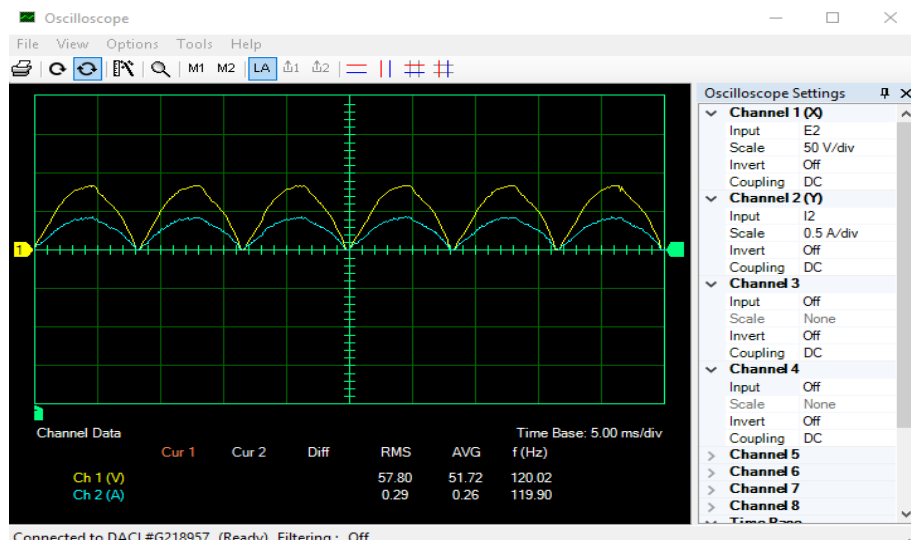


Figure 3: V_{out} vs I_{out} for $200\ \Omega$

2.1.2 DC motor

Input voltage vs the input current waveform for the DC motor is given in the following figure.

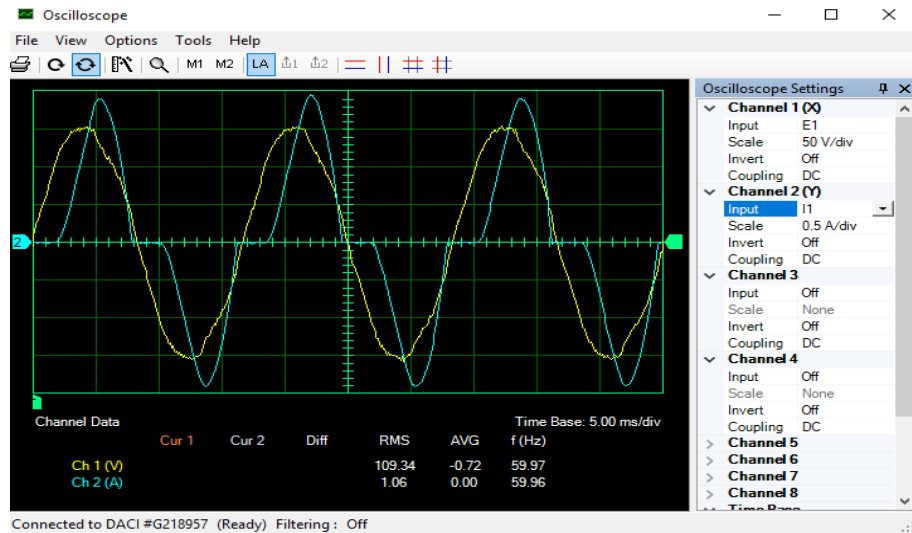


Figure 4: V_{in} vs I_{in} for DC motor

Output voltage vs the output current waveform for the DC motor is given in the following figure.

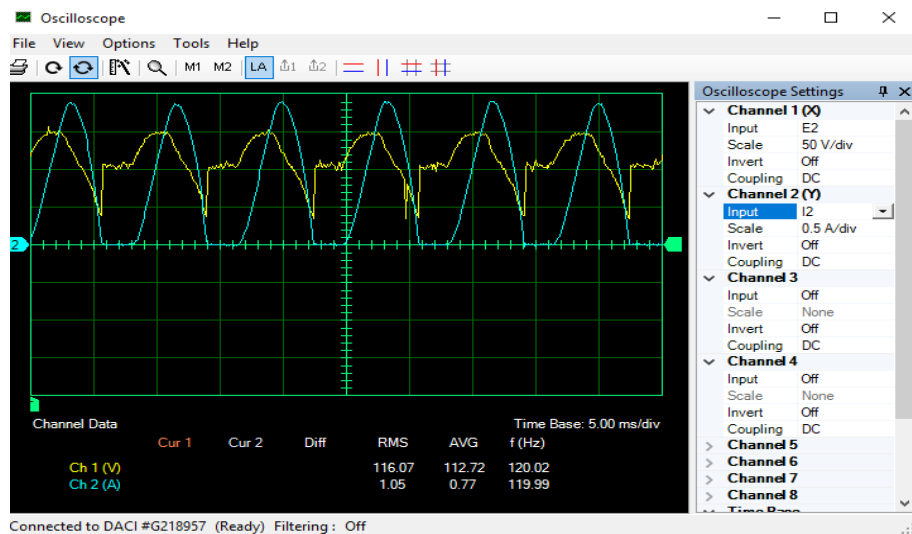


Figure 5: V_{out} vs I_{out} for DC motor

2.2 Harmonic Analysis of the waveforms

2.2.1 $200\ \Omega$

Harmonic analysis for the input voltage in the case of $200\ \Omega$

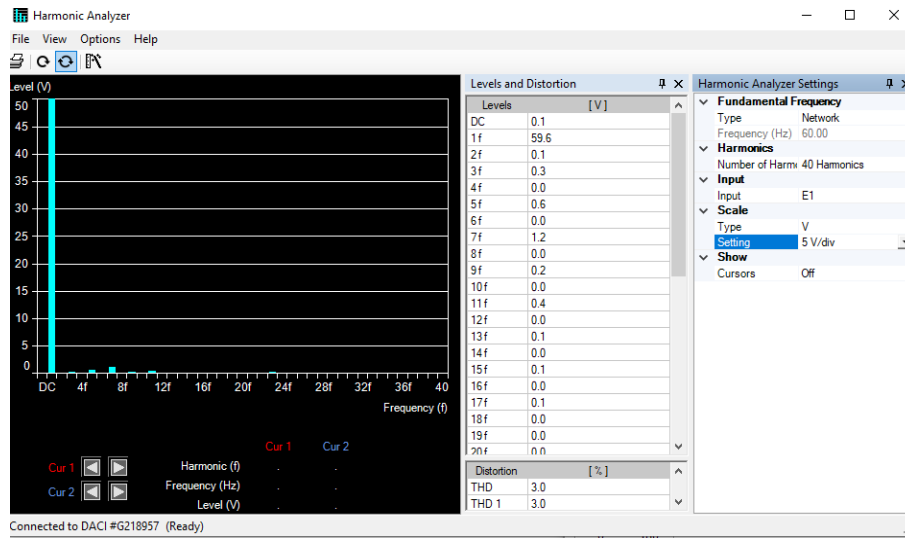


Figure 6: V_{in} Harmonics for $200\ \Omega$

Harmonic analysis for the output voltage in the case of $200\ \Omega$

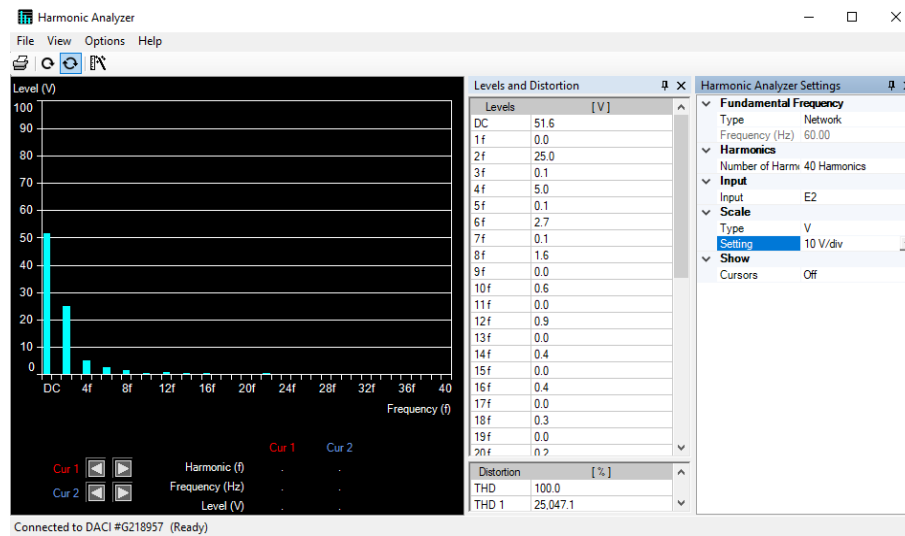


Figure 7: V_{out} Harmonics for $200\ \Omega$

Harmonic analysis for the input current in the case of $200\ \Omega$

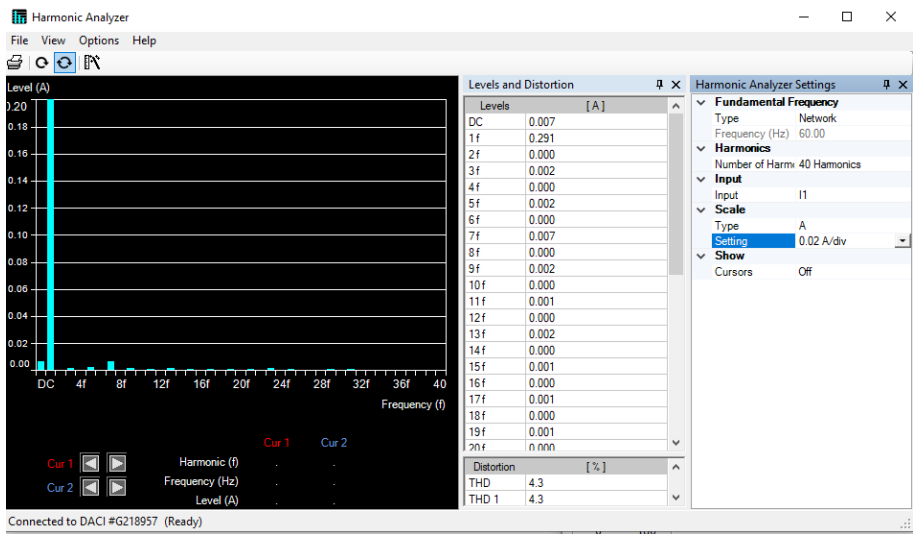


Figure 8: I_{in} Harmonics for $200\ \Omega$

Harmonic analysis for the output current in the case of $200\ \Omega$

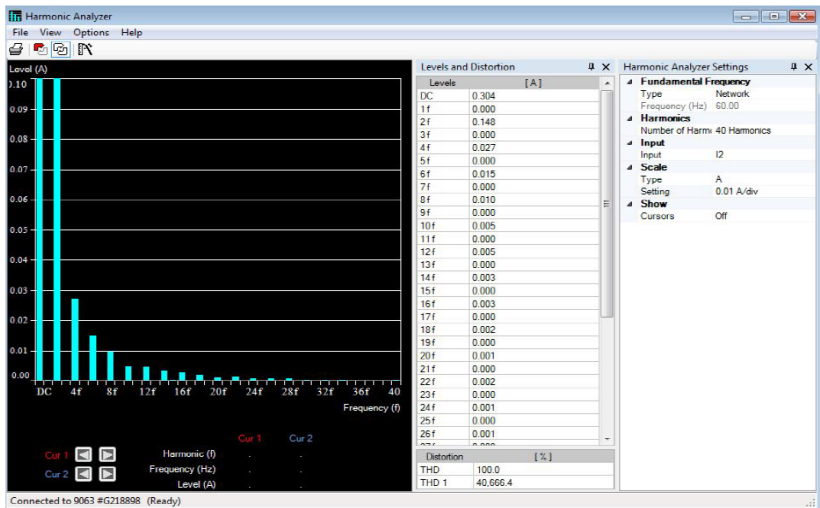


Figure 9: I_{out} Harmonics for $200\ \Omega$

2.2.2 DC motor

Harmonic analysis for the input voltage in the case of DC motor

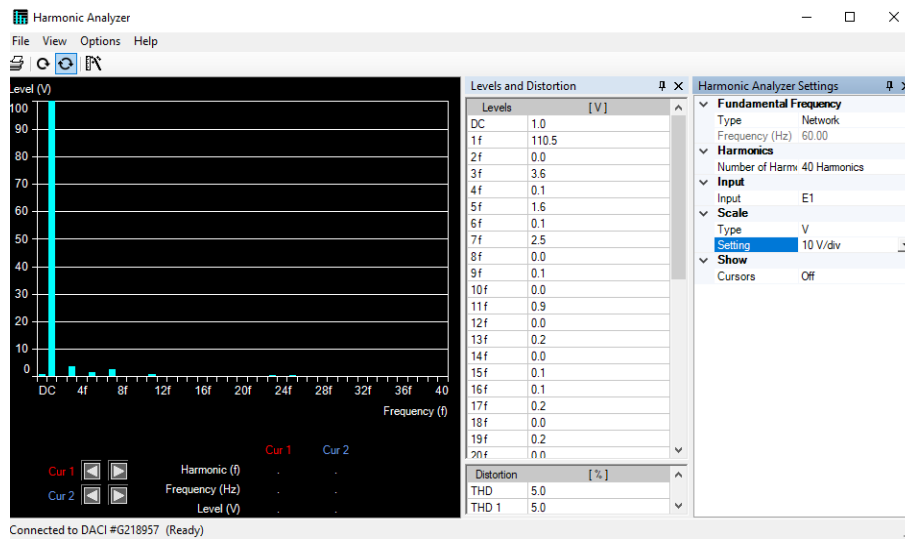


Figure 10: V_{in} Harmonics for DC motor

Harmonic analysis for the output voltage in the case of DC motor

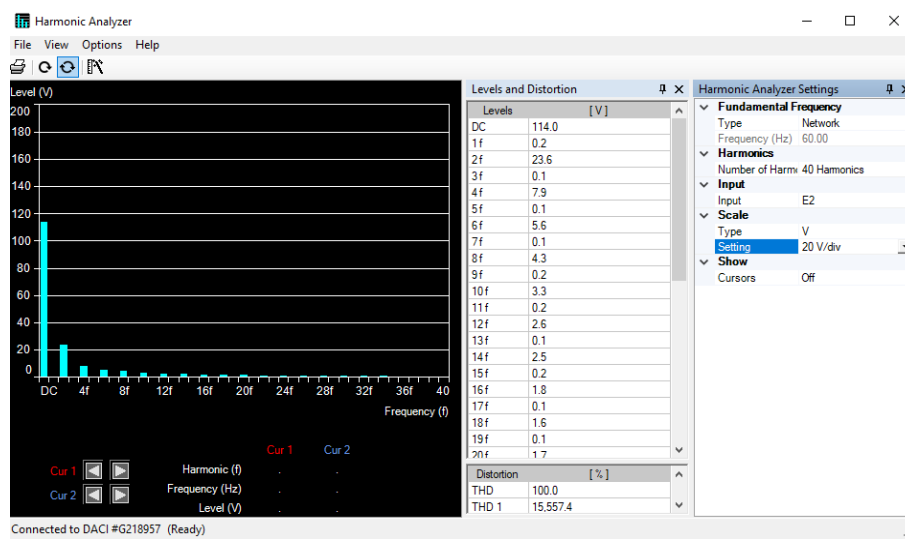


Figure 11: V_{out} Harmonics for DC motor

Harmonic analysis for the input current in the case of DC motor

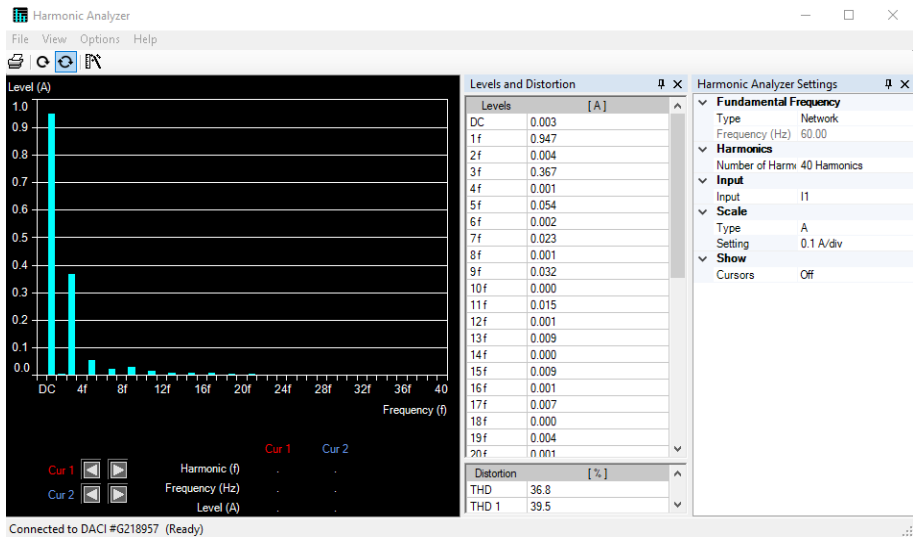


Figure 12: I_{in} Harmonics for DC motor

Harmonic analysis for the output current in the case of DC motor

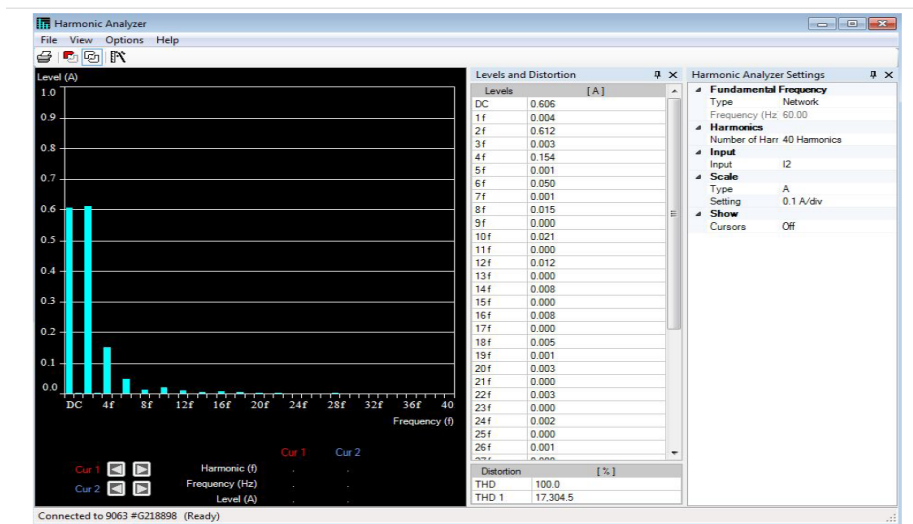


Figure 13: I_{out} Harmonics for DC motor

3 3ϕ full wave rectifier

The circuit for the 3ϕ full wave circuit is taken from the lab manual and given in the page below. The circuit is connected as shown in the figure below. Using the DAM we will monitor the input and output waveforms and harmonics of the voltage and load. The experiment will be conducted as the same as previous. It will be repeated for a $200\ \Omega$ and then later for a DC motor.

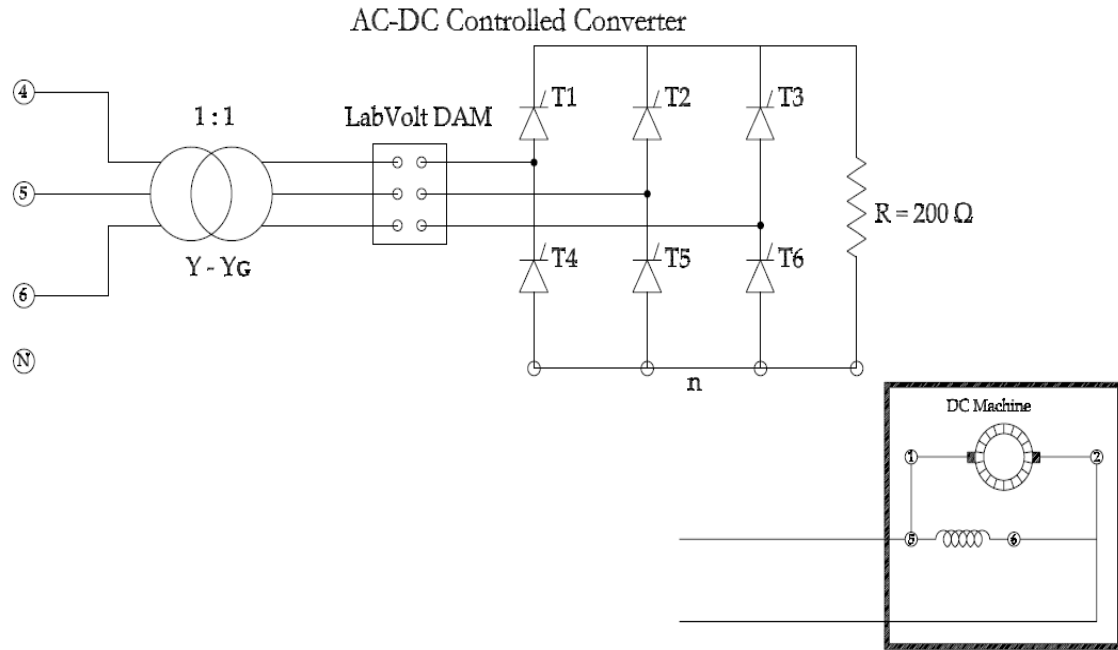


Figure 14: 3ϕ Full wave rectifier

3.1 Voltage and Current waveforms

3.1.1 200 Ω

Input voltage vs the input current waveform for the 3 ϕ circuit with the 200 Ω is given in the following figure.

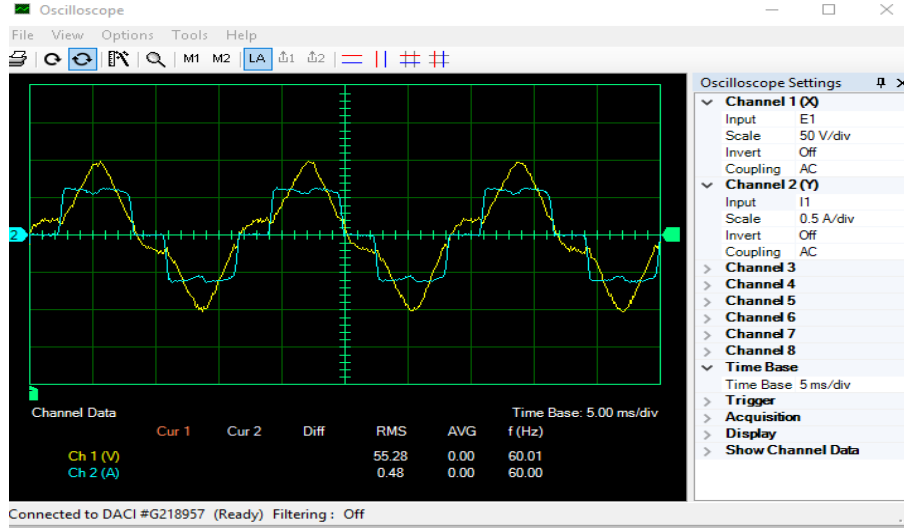


Figure 15: V_{in} vs I_{in} for 200 Ω

Output voltage vs the output current waveform for the 3 ϕ 200 Ω is given in the following figure.

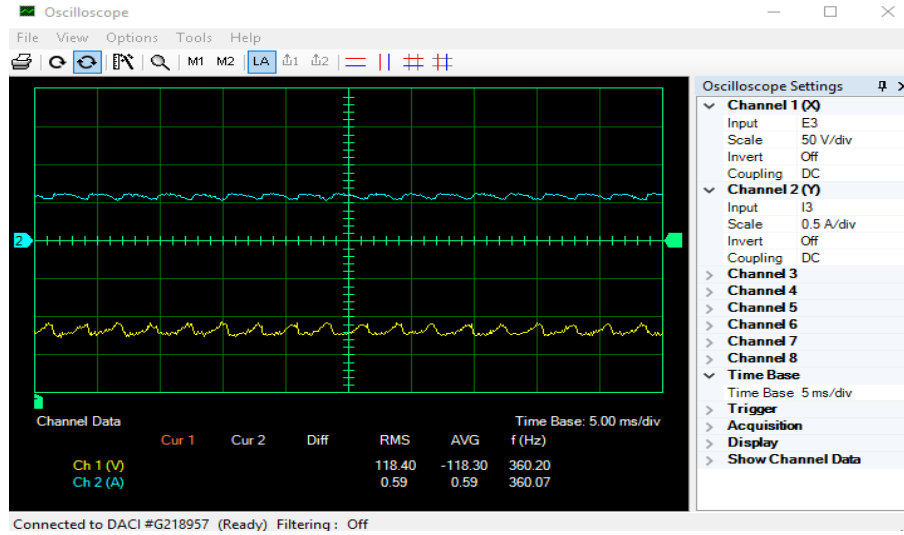


Figure 16: V_{out} vs I_{out} for 200 Ω

3.1.2 DC motor

Input voltage vs the input current waveform for the DC motor is given in the following figure.

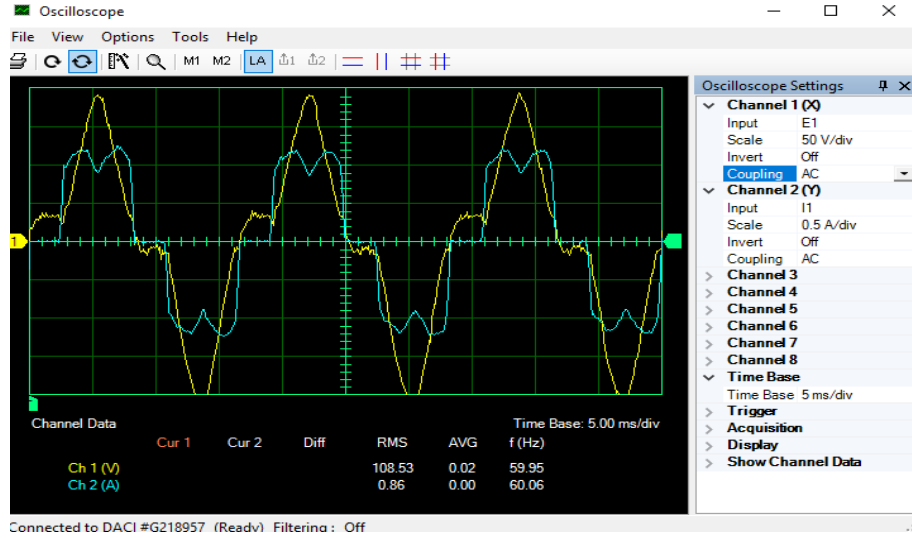


Figure 17: V_{in} vs I_{in} for DC motor

Output voltage vs the output current waveform for the DC motor is given in the following figure.

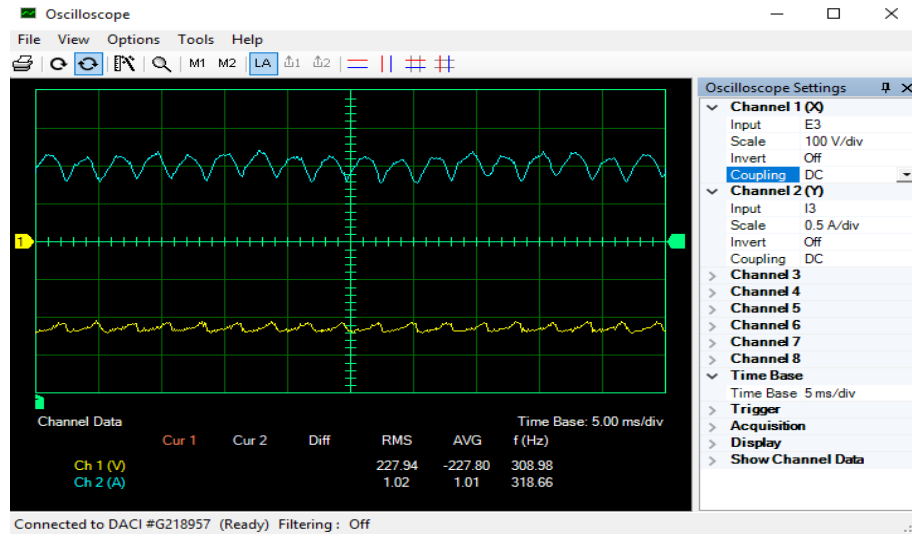


Figure 18: V_{out} vs I_{out} for DC motor

3.2 Harmonic Analysis of the waveforms

3.2.1 200 Ω

Harmonic analysis for the input voltage in the case of 200 Ω

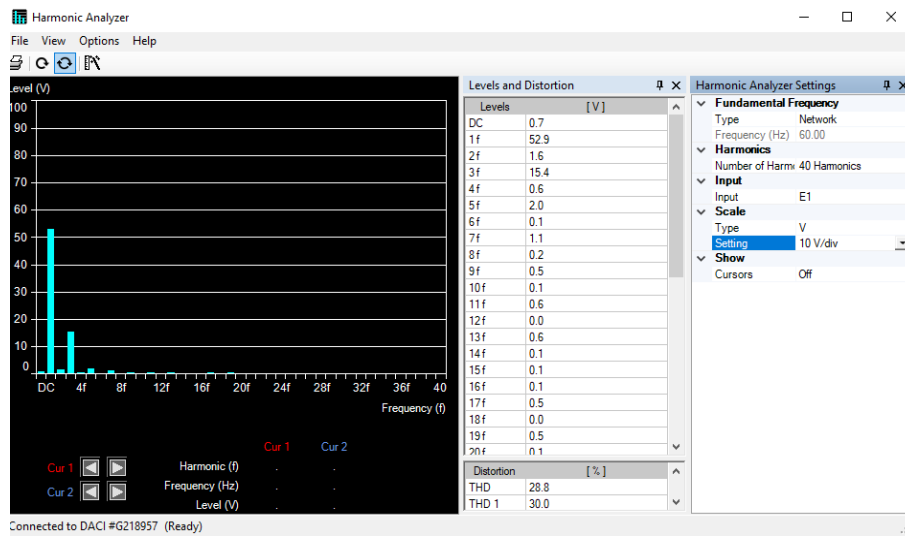


Figure 19: V_{in} Harmonics for 3ϕ 200 Ω

Harmonic analysis for the output voltage in the case of 200 Ω

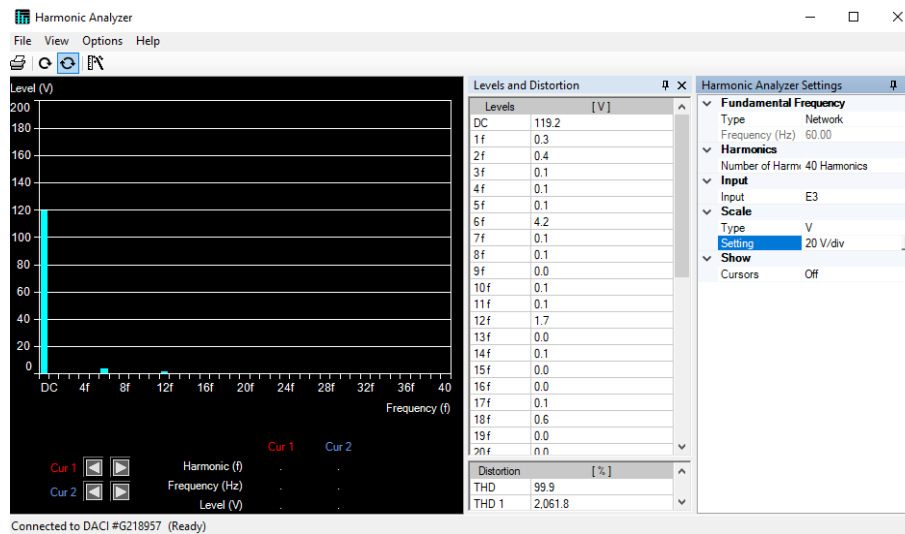


Figure 20: V_{out} Harmonics for 3ϕ 200 Ω

Harmonic analysis for the input current in the case of $200\ \Omega$

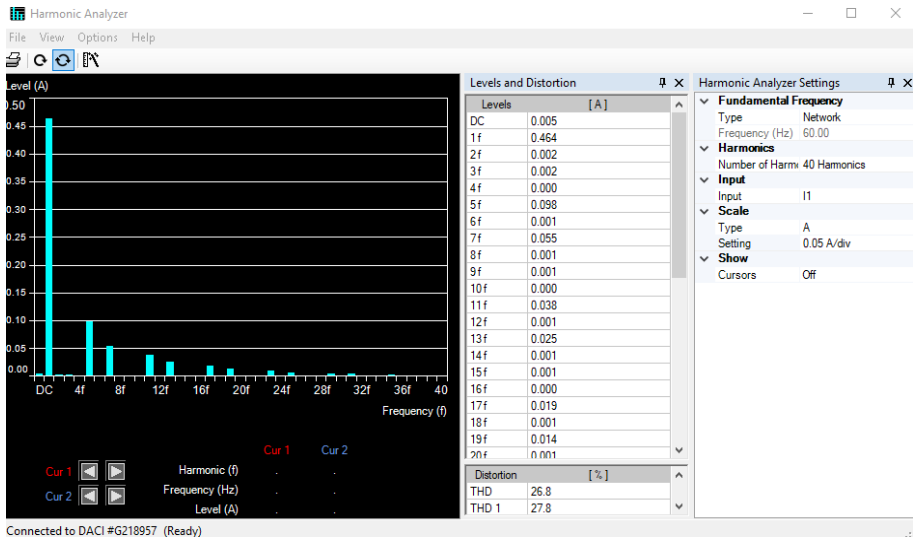


Figure 21: I_{in} Harmonics for $3\phi\ 200\ \Omega$

Harmonic analysis for the output current in the case of $200\ \Omega$

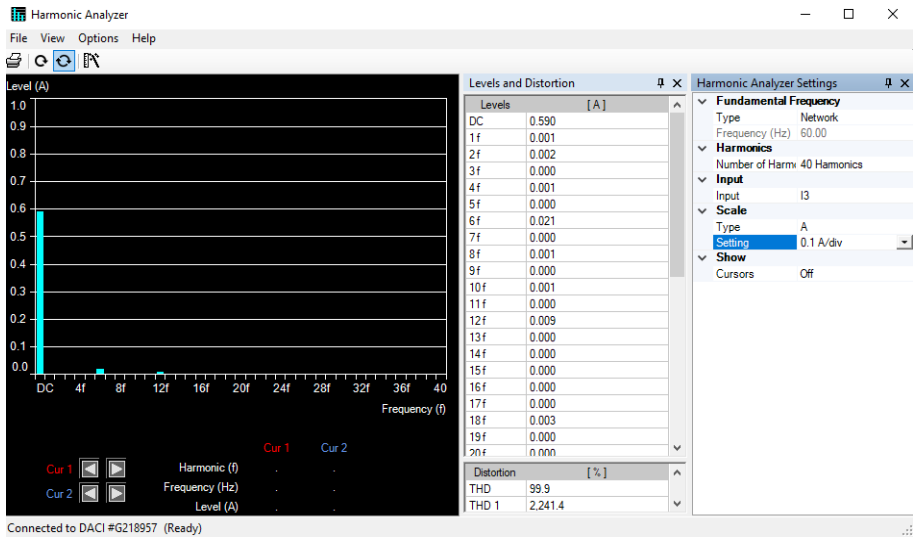


Figure 22: I_{out} Harmonics for $3\phi\ 200\ \Omega$

3.2.2 DC Motor

Harmonic analysis for the input voltage in the case of DC motor

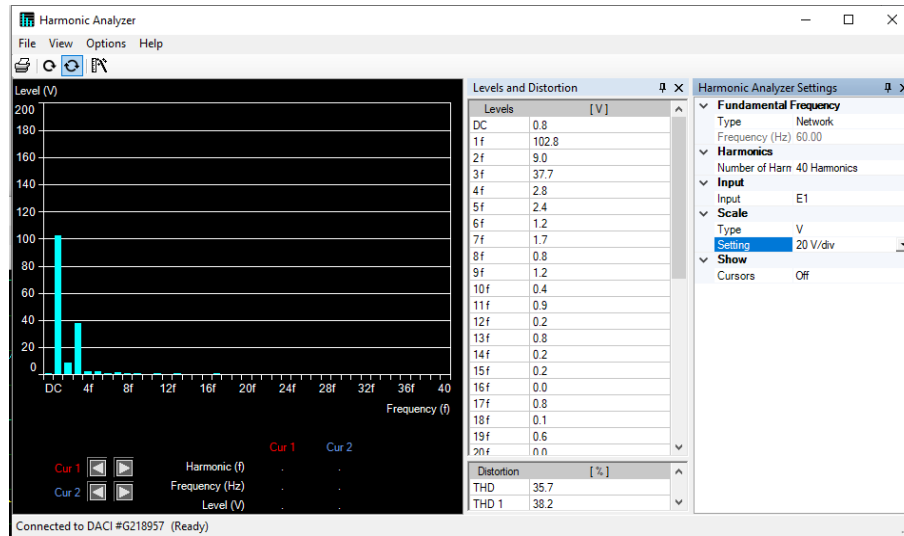


Figure 23: V_{in} Harmonics for 3 ϕ DC motor

Harmonic analysis for the output voltage in the case of DC motor

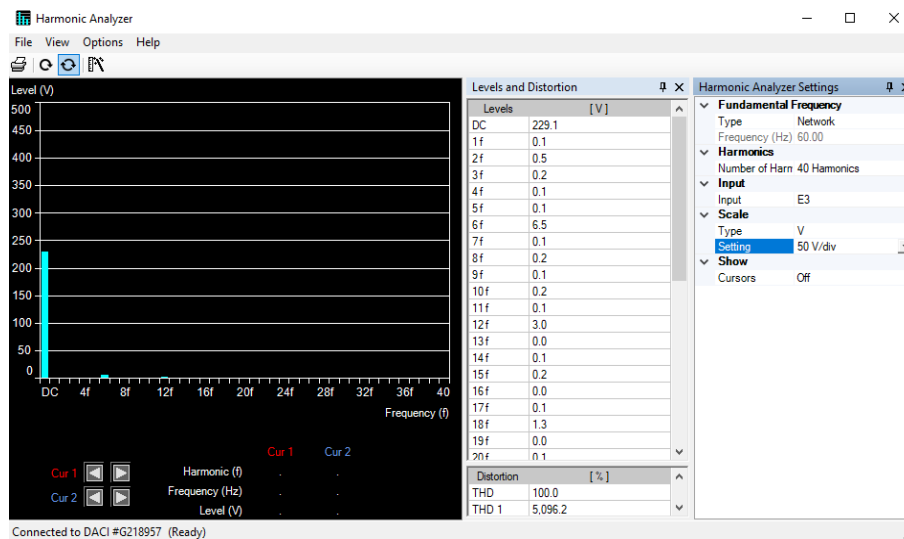


Figure 24: V_{out} Harmonics for 3 ϕ DC motor

Harmonic analysis for the input current in the case of DC motor

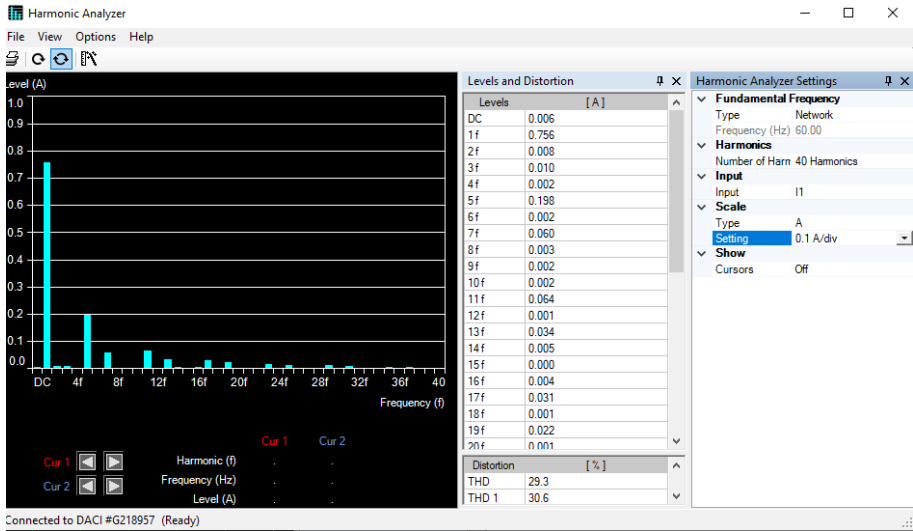


Figure 25: I_{in} Harmonics for 3 ϕ DC motor

Harmonic analysis for the output current in the case of DC motor

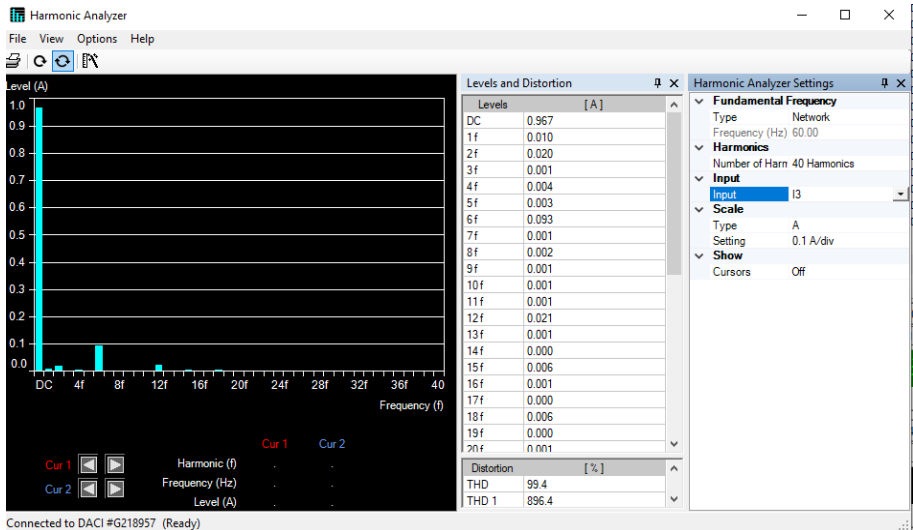


Figure 26: I_{out} Harmonics for 3 ϕ DC motor

4 Calculations and Questions

- Calculate the input power factor for both 1ϕ and 3ϕ converters for both load types.

Circuit	Load	P	Q	A	PF
1ϕ Converter	$200\ \Omega$	17.16	-0.2	17.17	0.9994
	DC motor	94.83	44.43	104.72	0.9055
3ϕ Converter	$200\ \Omega$	72.57	6.48	75.84	0.9568
	DC motor	228.93	18.24	229.65	0.9968

Table 1: Load power factor calculation

- Calculate the efficiency as : $\eta = \frac{P_{dc}}{P_{in}}$ for both the 1ϕ and 3ϕ load types

Type	Load	P_{dc}	P_{in}	η
1ϕ Converter	$200\ \Omega$	16.71	17.16	0.9737
	DC motor	90.00	94.83	0.9490
3ϕ Converter	$200\ \Omega$	69.62	72.57	0.9593
	DC motor	219.90	228.93	0.9605

Table 2: Load efficiency

- Compare the efficiency of the 1ϕ and 3ϕ rectifiers and comment on the impact of load type on the obtained efficiency values

The three phase rectifier is more efficient than the single phase. For both load types the three phase efficiency is higher than the single phase. For both loads the efficiency of the three phase converter is higher than that of the single phase with a $200\ \Omega$ load.

- Calculate the power losses for both the 1ϕ and 3ϕ load types

Type	Load	P_{dc}	P_{in}	P_{loss}
1ϕ Converter	$200\ \Omega$	16.71	17.16	0.45
	DC motor	90.00	94.83	4.83
3ϕ Converter	$200\ \Omega$	69.62	72.57	2.95
	DC motor	219.9	228.93	9.03

Table 3: Load power loss

5 Discussions and Conclusion

1 ϕ and 3 ϕ full wave rectifiers are individually tested in this experimental setup. Different types of voltages had different effects on the load setup of the experiment as the η of the whole system varied for the setup of the experiment. Increasing the voltage increased the efficiency of the experiment which is valid for the 3 ϕ full wave rectifier while for the 1 ϕ full wave rectifier it is not seen. From the table:3 it can be seen DC motor is having power losses which may origin from the motor core or due to the inductive behavior of the motor itself . We can see from the previous table:3 3 ϕ full wave rectifiers are more efficient than the 1 ϕ full wave rectifier in case of the DC motor . Switching the load to DC motor from the 200 Ω resistive load decreased the η for 1 ϕ . Based on the experiment we can tell that the η of the full wave rectifiers is related to the applied voltage and type of load supplied by the rectifier circuit.