



\_\_\_\_\_  
Grade Initials of Marker

**University of New Brunswick**  
**Dept. Of Electrical and Computer Engineering**  
**Room D41, Head Hall**

**LABORATORY/ASSIGNMENT/REPORT**  
**COVER PAGE**

Course#: ECE 4643 Experiment/Assignment#: Lab 1  
Course Instructor: Dr. Saleh Saleh Date: 09 October, 2019

Title: AC-DC Uncontrolled Power Converters

Group # (if applicable): \_\_\_\_\_

3652104 / Majid Inanloo  
Stud. Name (print)

3643581 / Tolulope Oluibenger  
Stud. Name (print)

Name of Author:

Majid / Tolulope  
Stud. Name (print)

Signature of Author:

Majid Inanloo / Tolulope  
Stud. Name (signature)

Comments:

# Table of Contents

1 Objective of This Experiment.....	4
2 The One-Phase Full Wave Rectifier .....	4
2.1 200 Ohm Resistor .....	5
2.1.1 Waveforms of voltages and currents for 200 $\Omega$ load – 1 phase.....	5
2.1.2 Measures of active and reactive powers for 200 $\Omega$ - 1 phase .....	5
2.1.3 Harmonic spectrums of input current, output current and output voltage for 200 $\Omega$ – 1 phase .....	6
2.2 DC Motor .....	7
2.2.1 Waveforms of voltages and currents for DC motor – 1 phase.....	7
2.2.2 Measures of active and reactive powers for DC motor - 1 phase .....	8
2.2.3 Harmonic spectrums of input current, output current and output voltage for the DC motor – 1 phase.....	8
3 The Three-Phase Full Wave Rectifier.....	10
3.1 200 Ohm Resistor .....	11
3.1.1 Waveforms of voltages and currents for 200 $\Omega$ load – 3 phase.....	11
3.1.2 Measures of active and reactive powers for 200 $\Omega$ - 3 phase .....	11
3.1.3 Harmonic spectrums of input current, output current and output voltage for 200 $\Omega$ – 3 phase .....	12
3.2 DC Motor .....	13
3.2.1 Waveforms of voltages and currents for DC motor – 3 phase.....	13
3.2.2 Measures of active and reactive powers for DC motor - 3 phase .....	14
3.2.3 Harmonic spectrums of input current, output current and output voltage for the DC motor– 3 phase.....	15
4 Calculations and Questions.....	16
4.1 Input Power Calculations.....	16

4.2 Efficiency Calculations .....	17
4.3 Efficiency Comparison .....	17
4.4 Power Losses Calculations .....	17
5 Conclusions.....	18

## List of Figures

Figure 1:- The figure shows a one phase full-wave rectifier and both load types .....	4
Figure 2:- The figure shows the waveforms of the input/output voltage and current for the 200 $\Omega$ resistor - 1phase .....	5
Figure 3:- The figures on the left and right shows the input/output of the active and reactive power respectively, for the 200 $\Omega$ resistor.....	5
Figure 4:- The figure shows the harmonics of input current for 200 $\Omega$ load - 1phase .....	6
Figure 5:- The figure shows the harmonics of output current for 200 $\Omega$ load - 1phase .....	6
Figure 6:- The figure shows the harmonics of output voltage for 200 $\Omega$ load - 1phase .....	7
Figure 7:- The figure shows the waveforms of the input/output voltage and current for the DC motor - 1phase.....	7
Figure 8:- The figures on the left and right shows the input/output of the active and reactive power respectively, for the DC motor.....	8
Figure 9:- The figure shows the harmonics of the input current for the DC motor - 1phase .....	8
Figure 10:- The figure shows the harmonics of the output current for the DC motor - 1phase .....	9
Figure 11:- The figure shows the harmonics of the output voltage for the DC motor - 1phase .....	9
Figure 12:- The figure shows a three phase full-wave rectifier and both load types.....	10
Figure 13:- The figure shows the waveforms of the input/output voltage and current for the 200 $\Omega$ resistor – 3 phase.....	11
Figure 14:- The figures on the left and right shows the input/output of the active and reactive power respectively, for the 200 $\Omega$ resistor.....	11
Figure 15:- The figure shows the harmonics of input current for 200 $\Omega$ load – 3 phase.....	12
Figure 16:- The figure shows the harmonics of output current for 200 $\Omega$ load – 3 phase.....	12

Figure 17:- The figure shows the harmonics of output voltage for 200 $\Omega$ load – 3 phase .....	13
Figure 18:- The figure shows the waveforms of the input voltage and current for the DC motor – 3 phase .....	13
Figure 19:- The figure shows the waveforms of the output voltage and current for the DC motor – 3 phase .....	14
Figure 20:- The figures on the left and right shows the input/output of the active and reactive power respectively, for the DC motor.....	14
Figure 21:- The figure shows the harmonics of the input current for the DC motor – 3 phase....	15
Figure 22:- The figure shows the harmonics of the output current for the DC motor – 3 phase..	15
Figure 23:- The figure shows the harmonics of the output voltage for the DC motor – 3 phase .	16

## List of Tables

Table 1:- The table shows the calculations for the input power factor .....	16
Table 2:- The table shows the calculations for the efficiency .....	17
Table 3:- The table shows the calculations of the Power Losses .....	18

## 1 Objective of This Experiment

The aim of this experiment was to examine the performance of the single and three phase full wave rectifiers when supplying to different load types. The performance measures considered include; the harmonics on the input/output side of the converter, the input power factor, and the efficiency of the tested AC-DC rectifiers.

## 2 The One-Phase Full Wave Rectifier

The figure below shows the circuit for the one phase full wave rectifier. For this experiment, we used the data acquisition module (DAM) to observe and record; the input/output currents, input/output voltages, and the active & reactive power. Due to the rectifiers used in the rectification process, we will observe different harmonics for the input/output currents and voltages. First, the experiment was conducted using a 200 ohm resistor with an input voltage 60V; then the resistor was replaced using a DC motor with an input voltage 110V. By setting the firing angle to zero ( $\alpha=0$ ) the rectifier behaves like a diode.

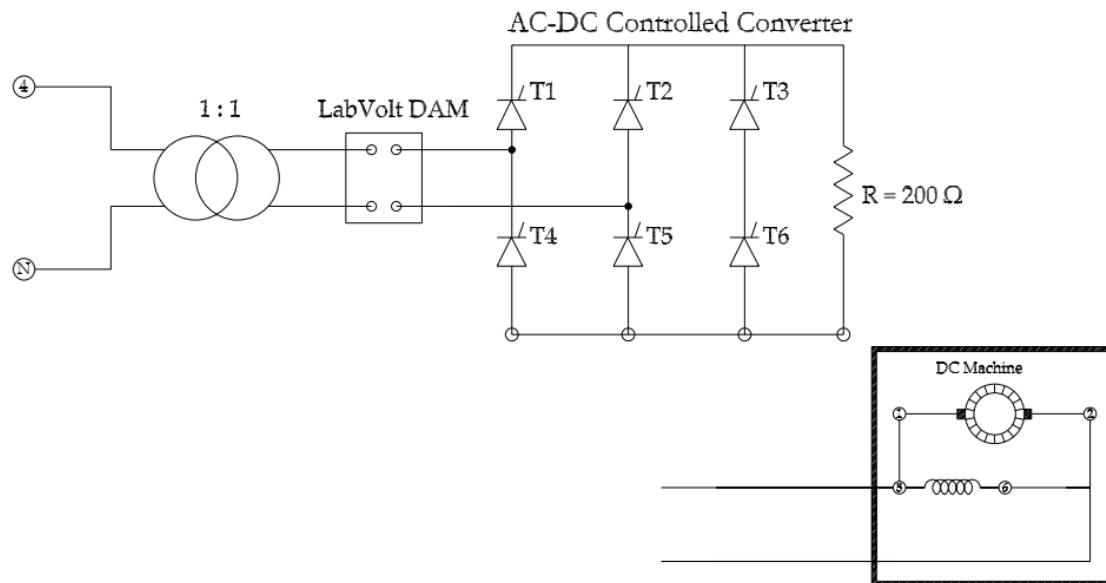


Figure 1:- The figure shows a one phase full-wave rectifier and both load types

## 2.1 200 Ohm Resistor

### 2.1.1 Waveforms of voltages and currents for 200 $\Omega$ load – 1 phase

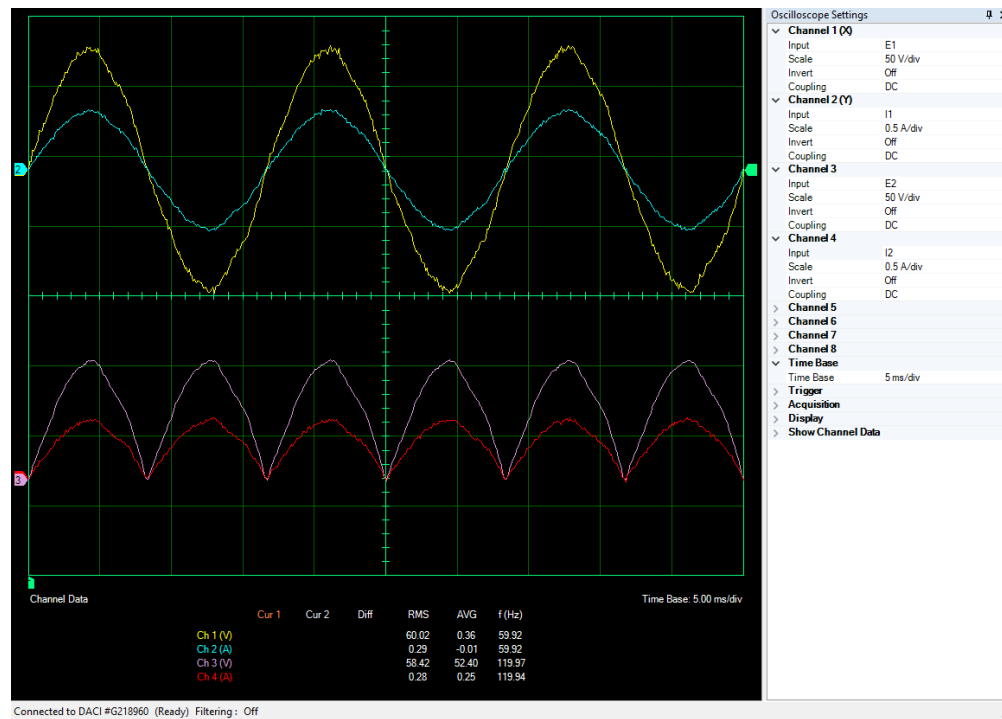


Figure 2:- The figure shows the waveforms of the input/output voltage and current for the 200  $\Omega$  resistor - 1phase

### 2.1.2 Measures of active and reactive powers for 200 $\Omega$ - 1 phase

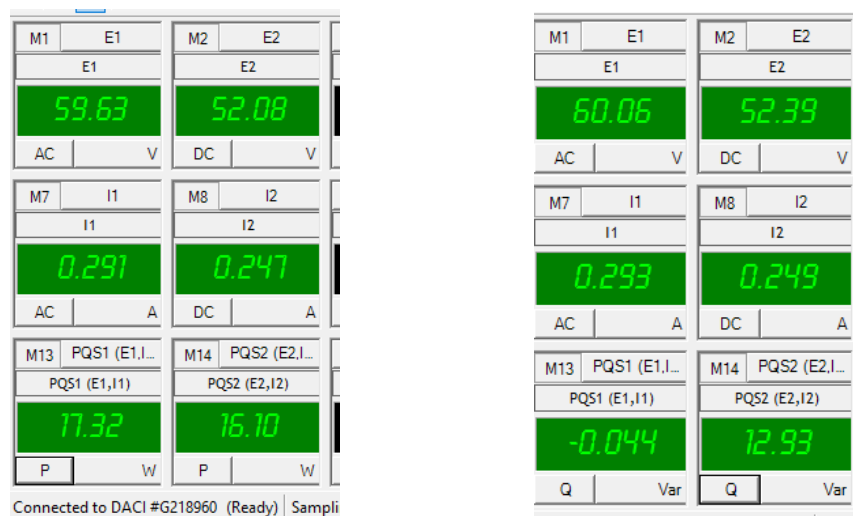


Figure 3:- The figures on the left and right shows the input/output of the active and reactive power respectively, for the 200  $\Omega$  resistor.

### 2.1.3 Harmonic spectrums of input current, output current and output voltage for 200 $\Omega$ – 1 phase

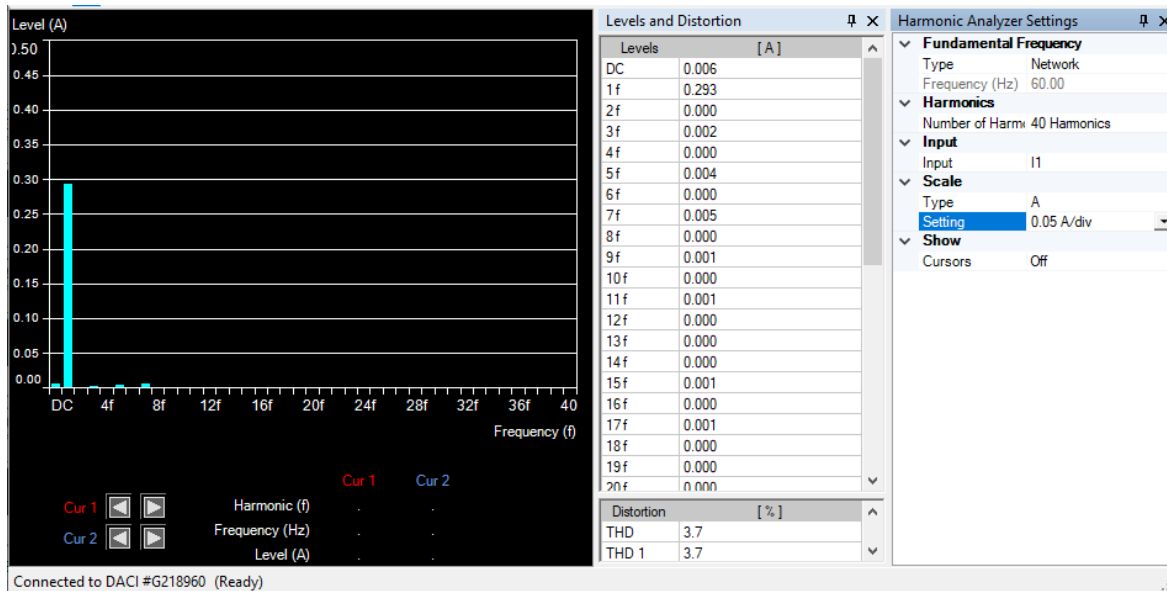


Figure 4:- The figure shows the harmonics of input current for 200  $\Omega$  load - 1phase

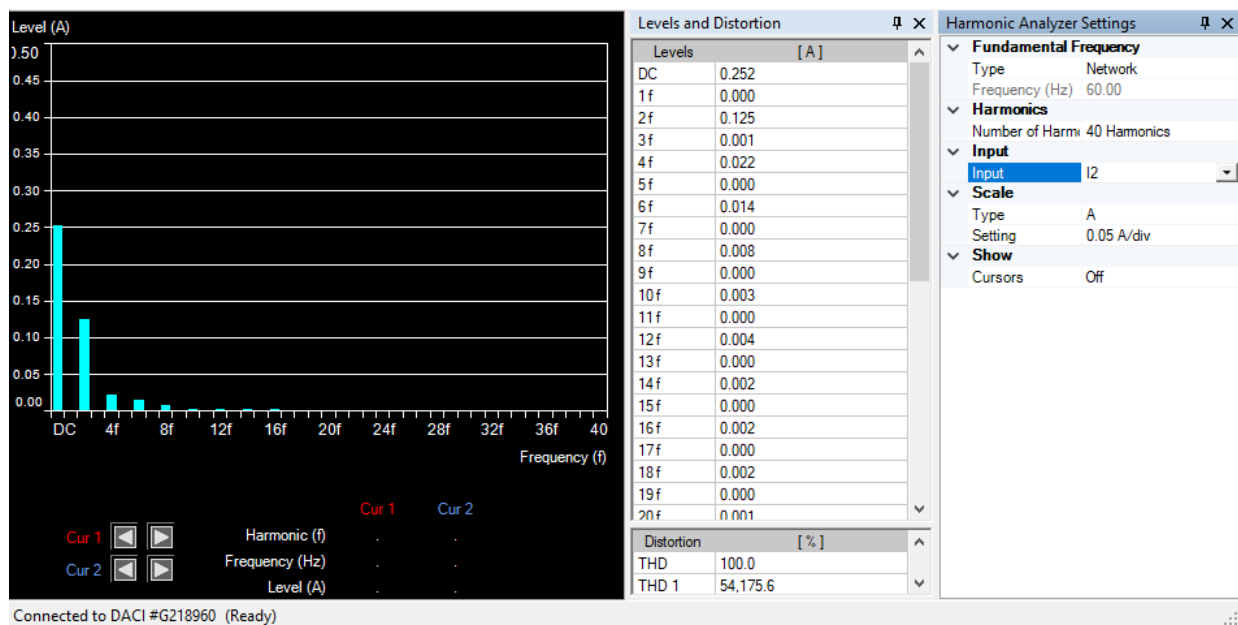


Figure 5:- The figure shows the harmonics of output current for 200  $\Omega$  load - 1phase

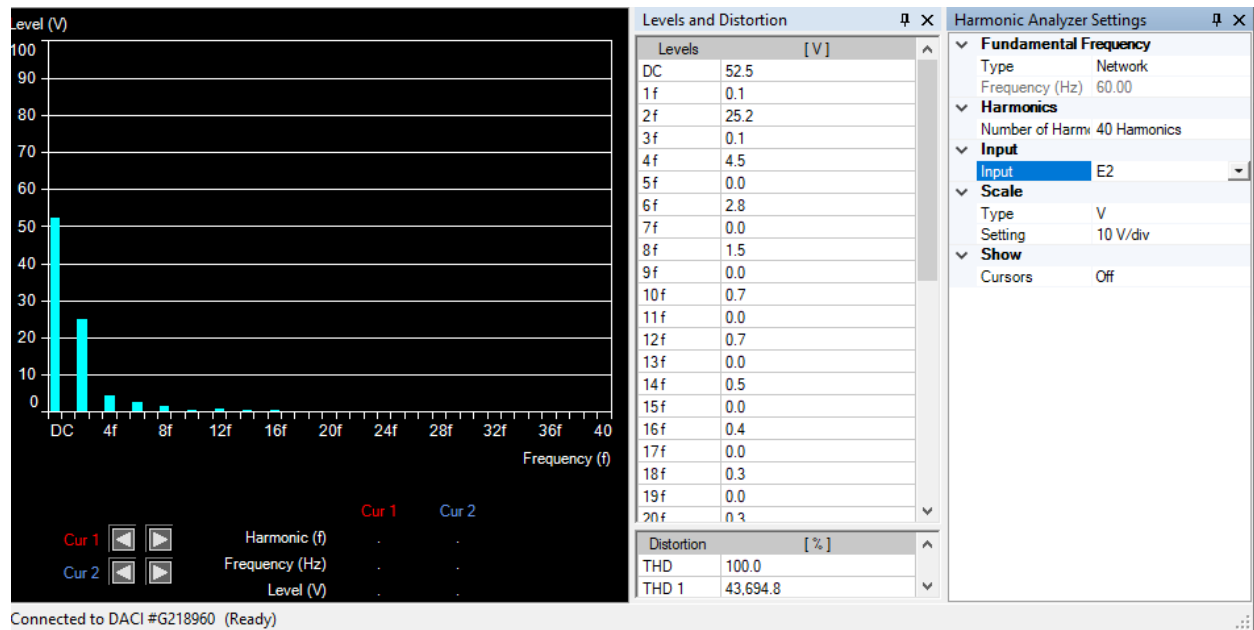


Figure 6:- The figure shows the harmonics of output voltage for 200  $\Omega$  load - 1phase

## 2.2 DC Motor

### 2.2.1 Waveforms of voltages and currents for DC motor – 1 phase

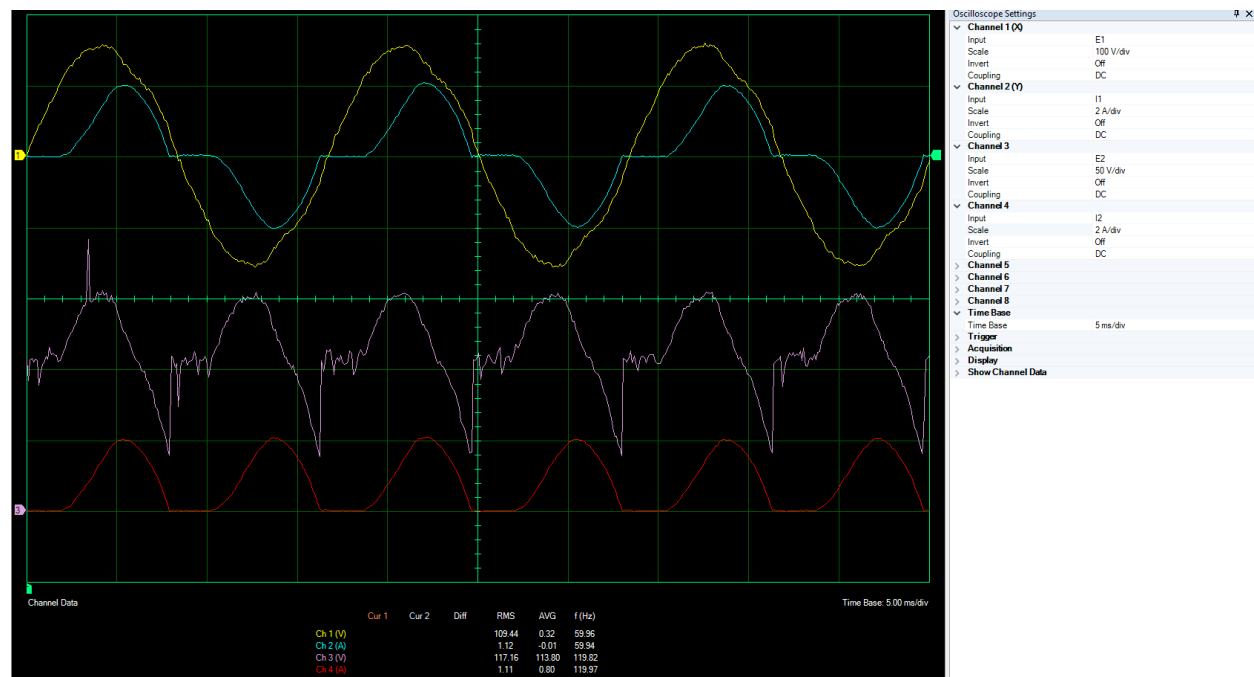


Figure 7:- The figure shows the waveforms of the input/output voltage and current for the DC motor - 1phase



## 2.2.2 Measures of active and reactive powers for DC motor - 1 phase

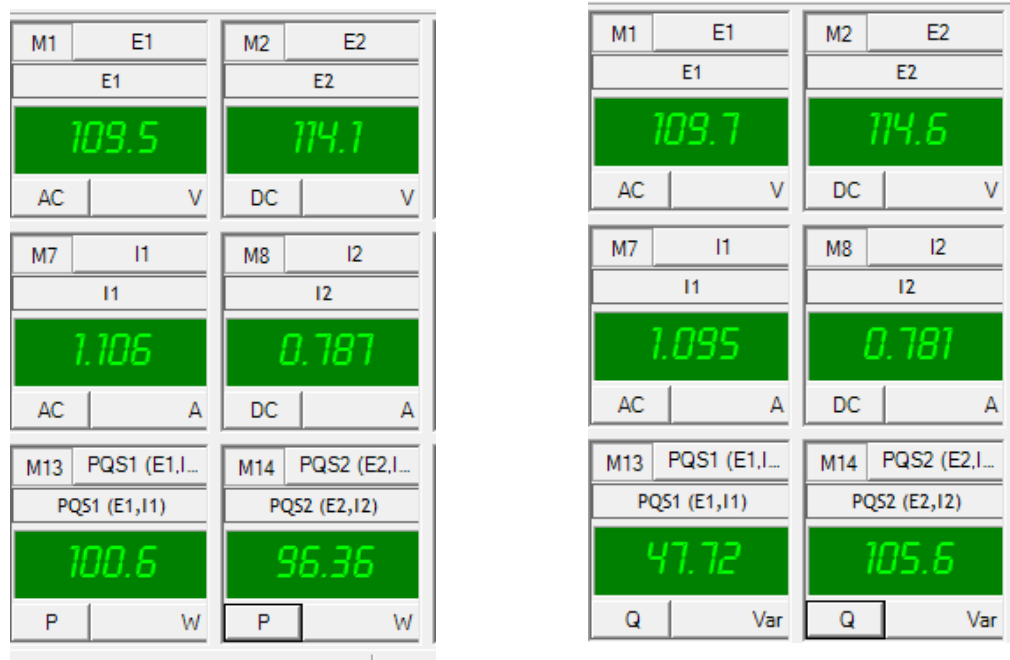


Figure 8:- The figures on the left and right shows the input/output of the active and reactive power respectively, for the DC motor.

## 2.2.3 Harmonic spectrums of input current, output current and output voltage for the DC motor – 1 phase

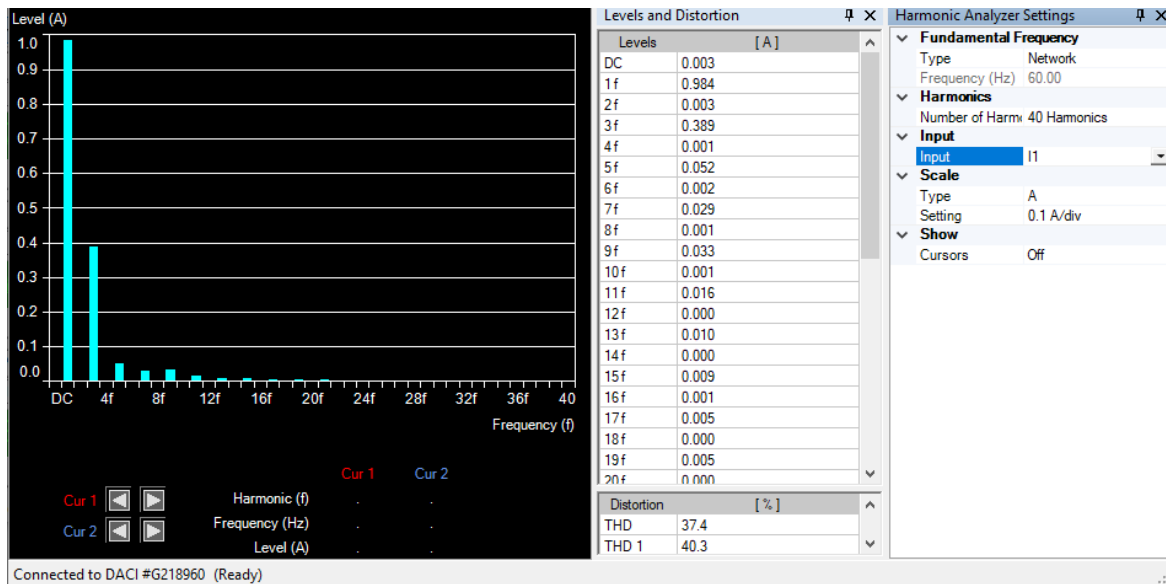


Figure 9:- The figure shows the harmonics of the input current for the DC motor - 1phase

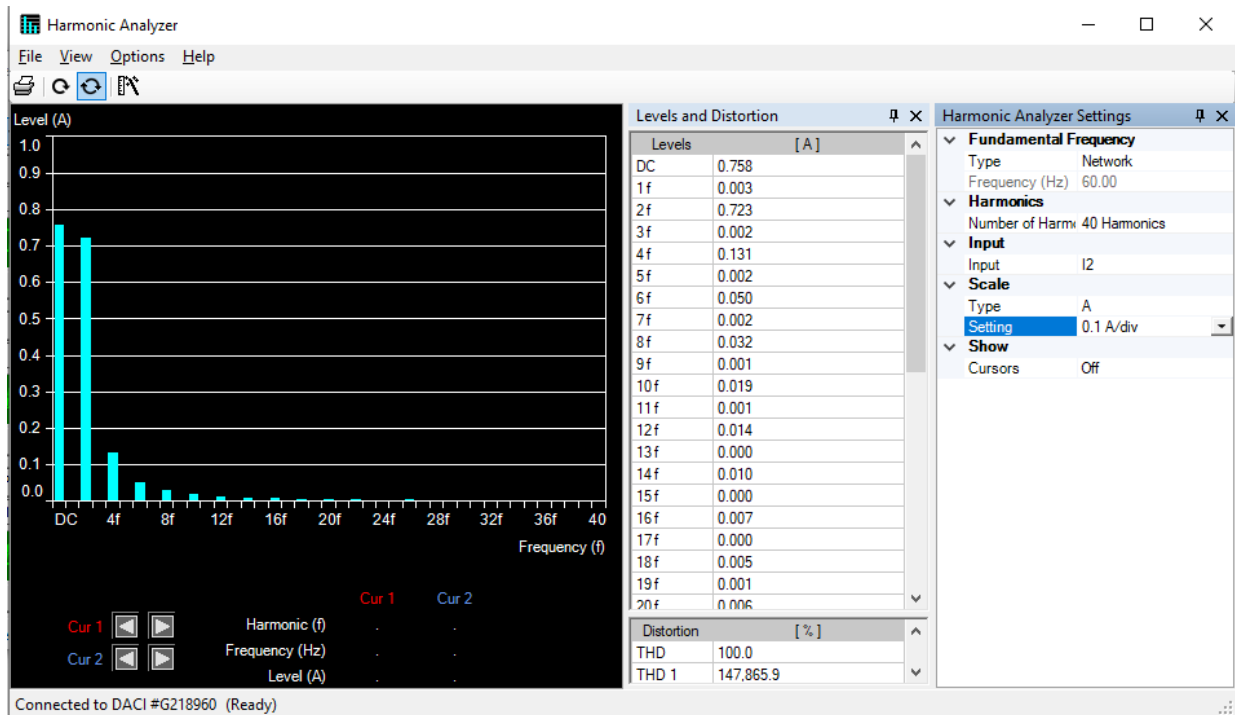


Figure 10:- The figure shows the harmonics of the output current for the DC motor - 1phase

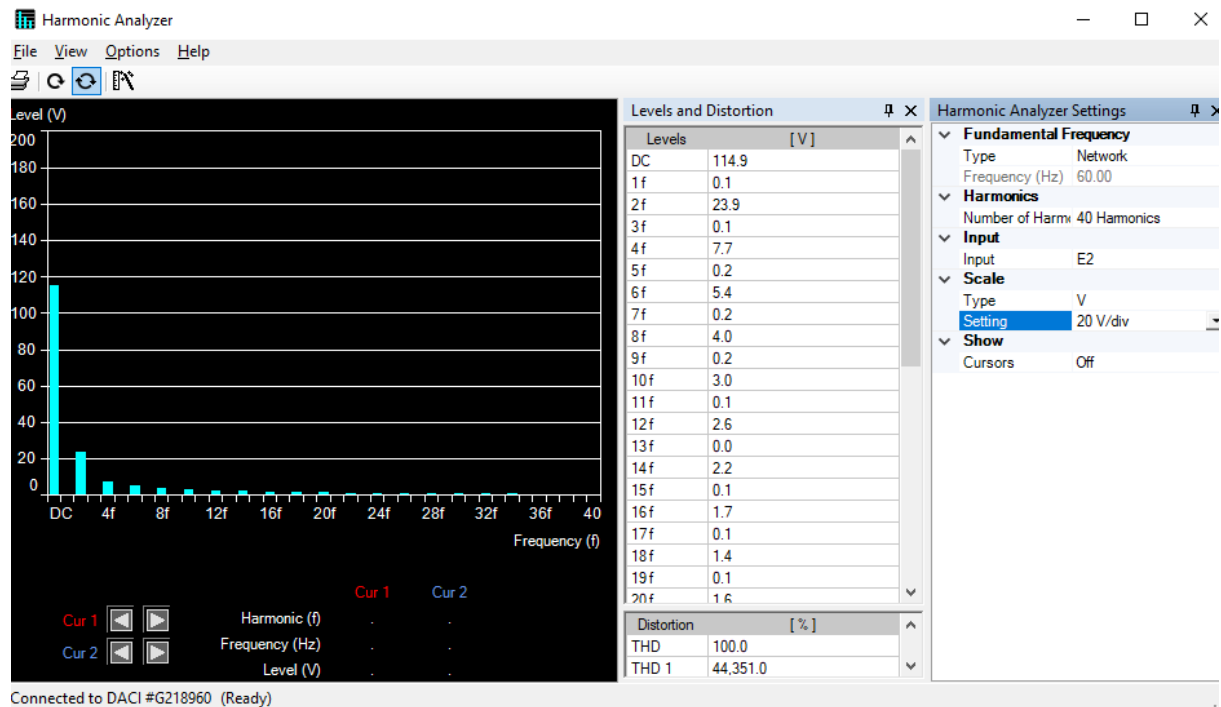


Figure 11:- The figure shows the harmonics of the output voltage for the DC motor - 1phase

### 3 The Three-Phase Full Wave Rectifier

The figure below shows the circuit for the three phase full wave rectifier. We used the data acquisition module (DAM) to observe and record; the input/output currents, input/output voltages, and the active & reactive power. First, the experiment was also conducted using a 200 ohm resistor with an input voltage 60V; then the resistor was replaced using a DC motor with an input voltage 110V. By setting the firing angle to zero ( $\alpha=0$ ) the rectifier behaves like a diode.

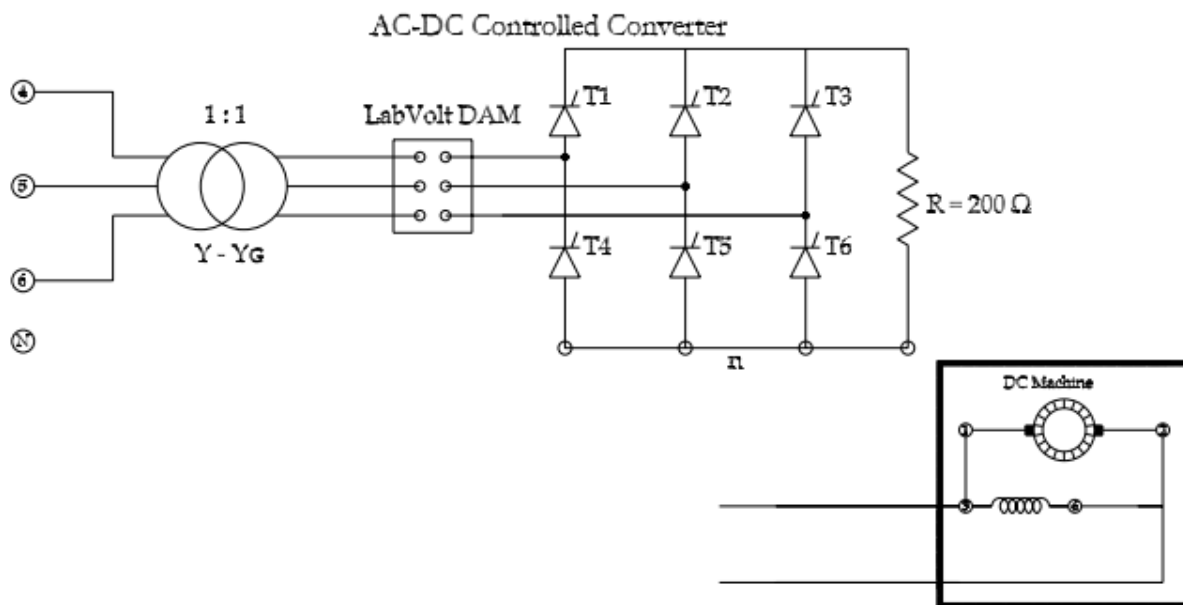


Figure 12:- The figure shows a three phase full-wave rectifier and both load types

### 3.1 200 Ohm Resistor

#### 3.1.1 Waveforms of voltages and currents for 200 $\Omega$ load – 3 phase

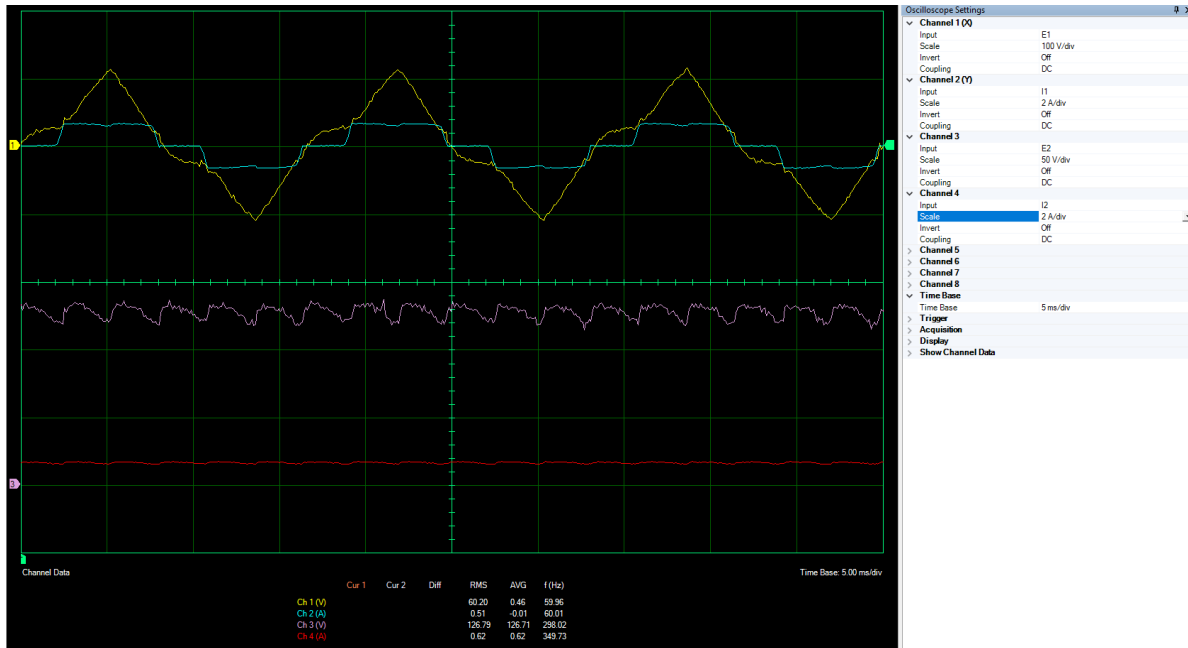


Figure 13:- The figure shows the waveforms of the input/output voltage and current for the 200  $\Omega$  resistor – 3 phase

#### 3.1.2 Measures of active and reactive powers for 200 $\Omega$ - 3 phase

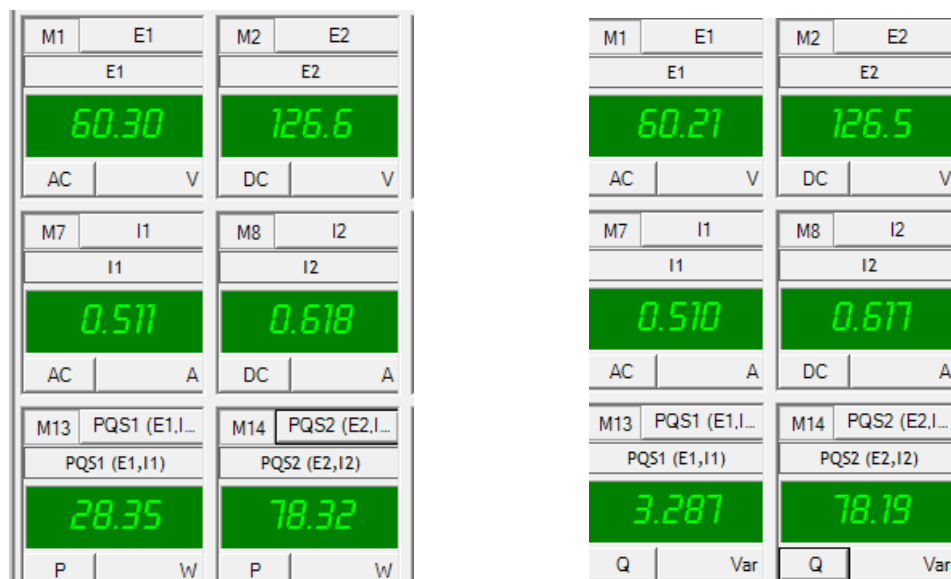


Figure 14:- The figures on the left and right shows the input/output of the active and reactive power respectively, for the 200  $\Omega$  resistor.

### 3.1.3 Harmonic spectrums of input current, output current and output voltage for 200 $\Omega$ – 3 phase

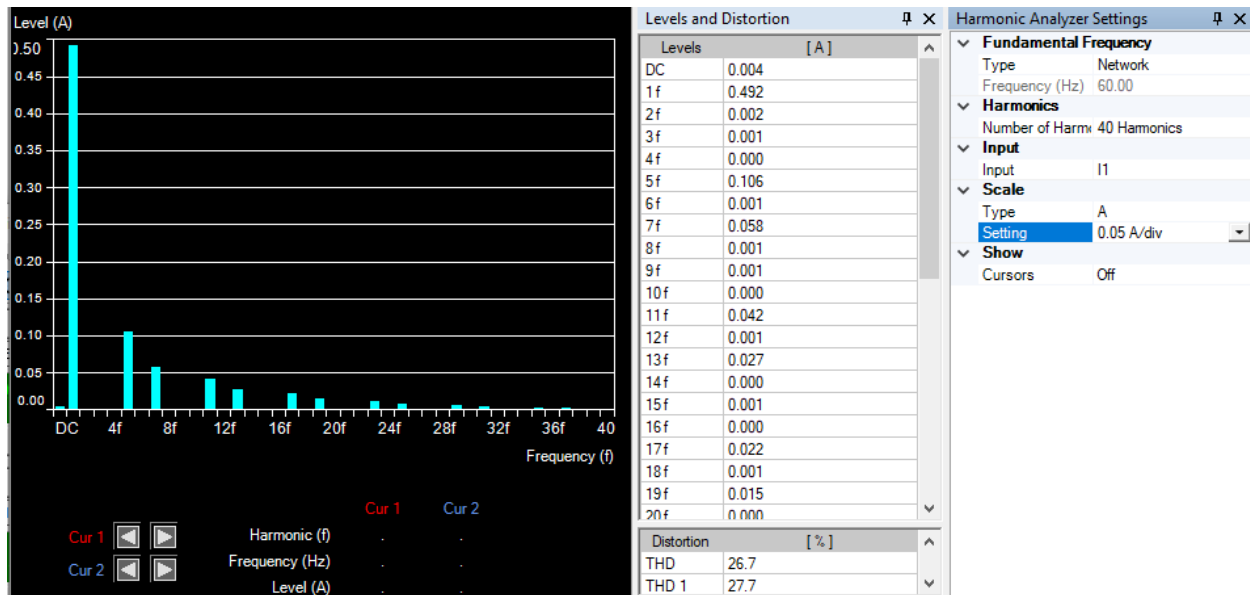


Figure 15:- The figure shows the harmonics of input current for 200  $\Omega$  load – 3 phase

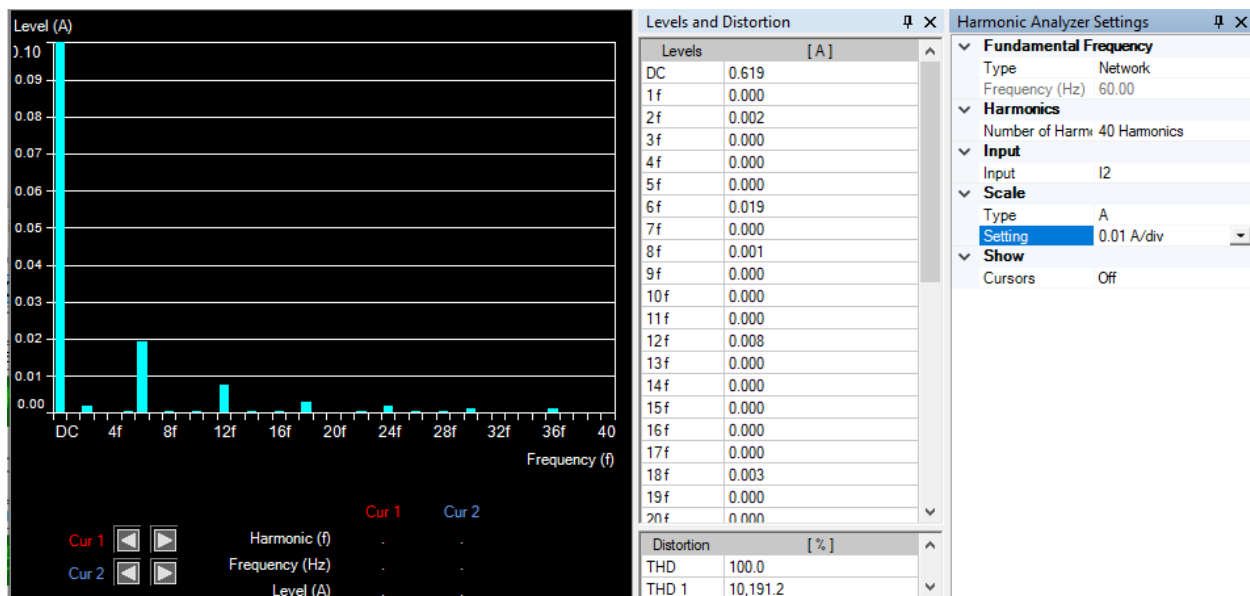


Figure 16:- The figure shows the harmonics of output current for 200  $\Omega$  load – 3 phase

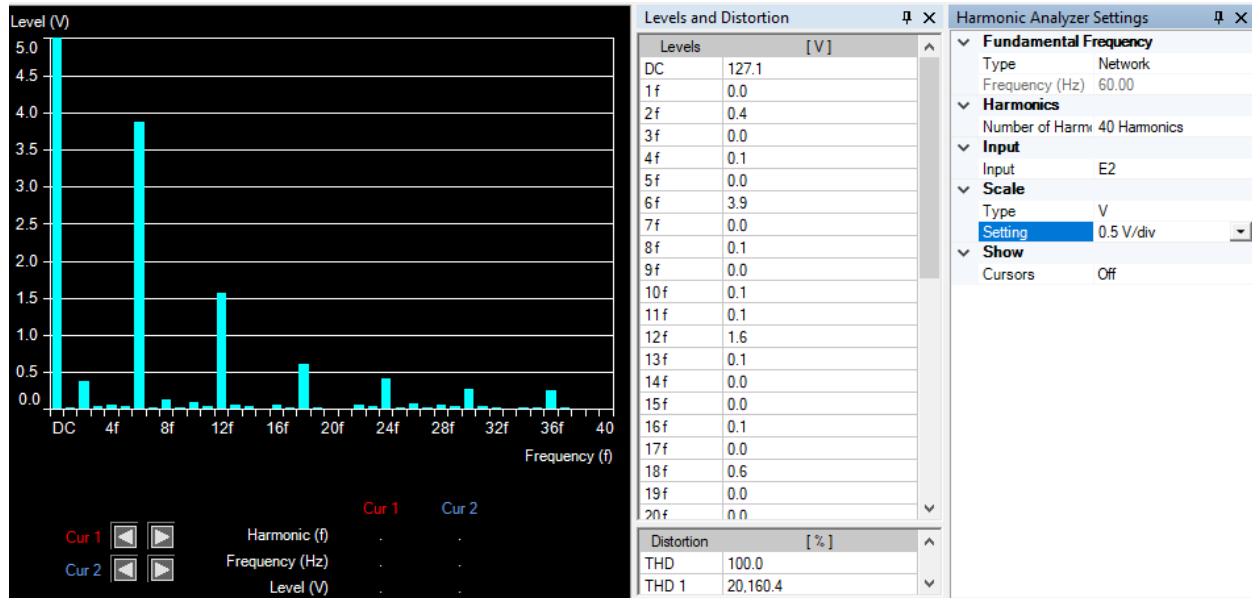


Figure 17:- The figure shows the harmonics of output voltage for 200  $\Omega$  load – 3 phase

## 3.2 DC Motor

### 3.2.1 Waveforms of voltages and currents for DC motor – 3 phase

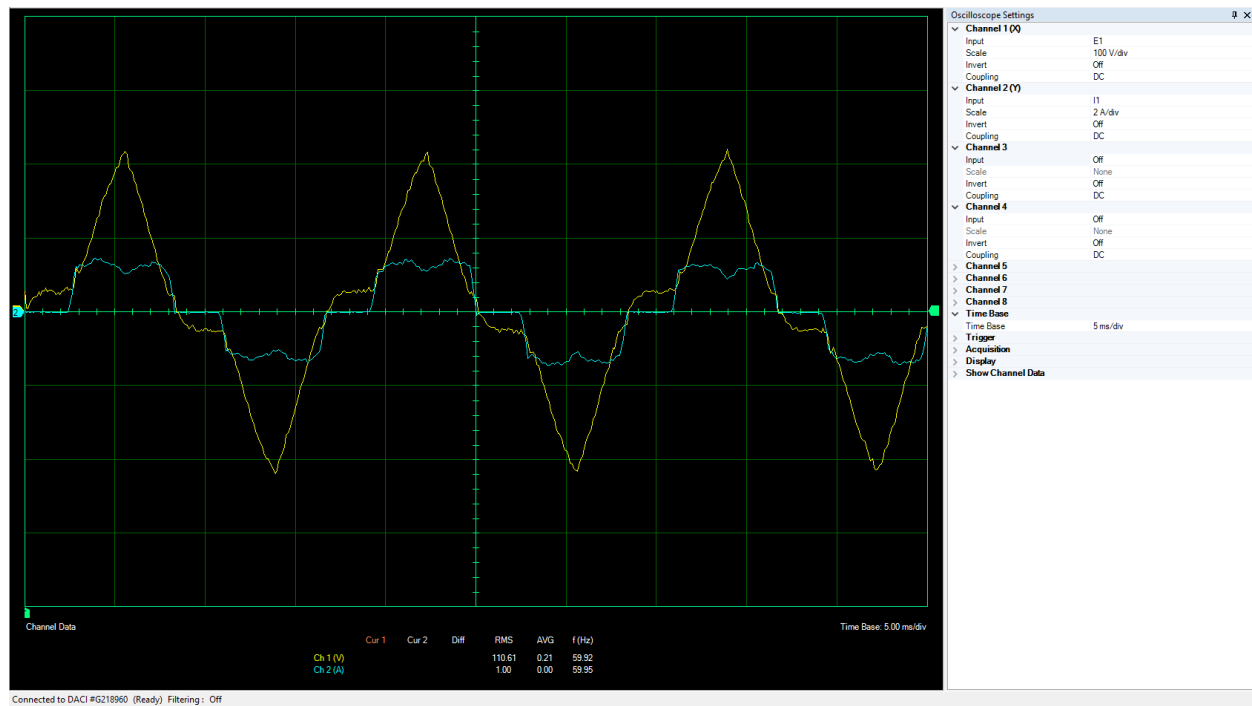


Figure 18:- The figure shows the waveforms of the input voltage and current for the DC motor – 3 phase



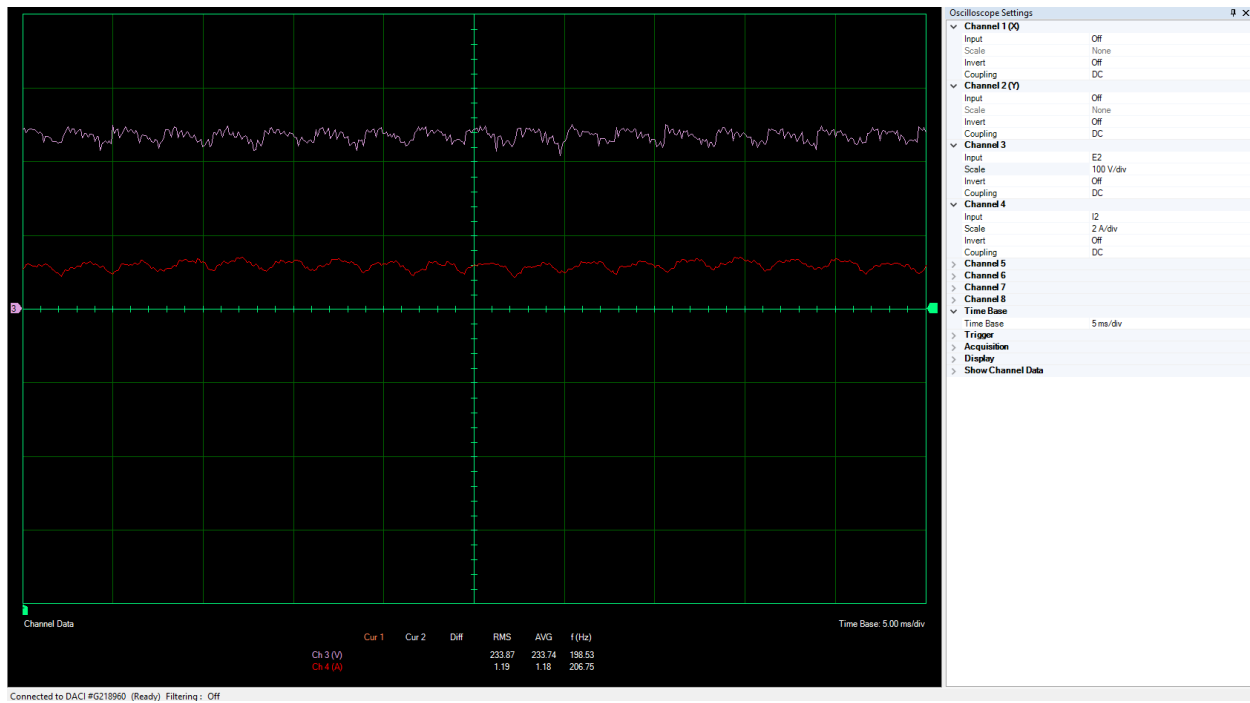


Figure 19:- The figure shows the waveforms of the output voltage and current for the DC motor – 3 phase
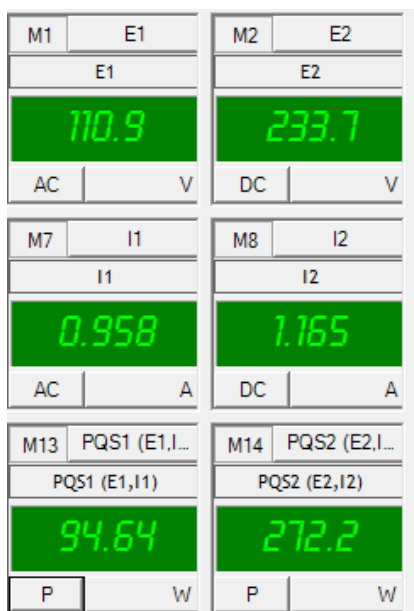
### 3.2.2 Measures of active and reactive powers for DC motor - 3 phase



Connected to DACI #G218960 (Ready) Samp

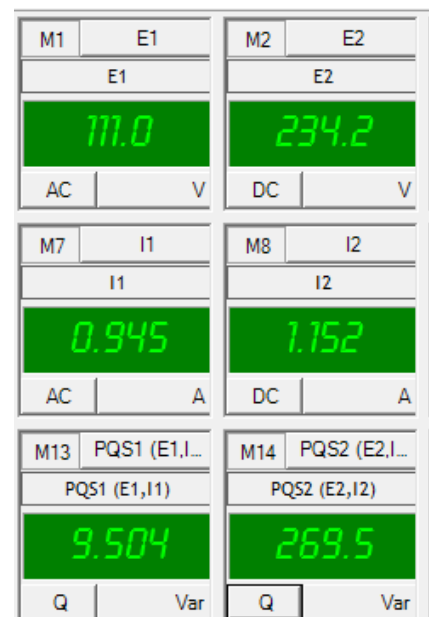

Connected to DACI #G218960 (Ready) Sampl

Figure 20:- The figures on the left and right shows the input/output of the active and reactive power respectively, for the DC motor.

### 3.2.3 Harmonic spectrums of input current, output current and output voltage for the DC motor– 3 phase

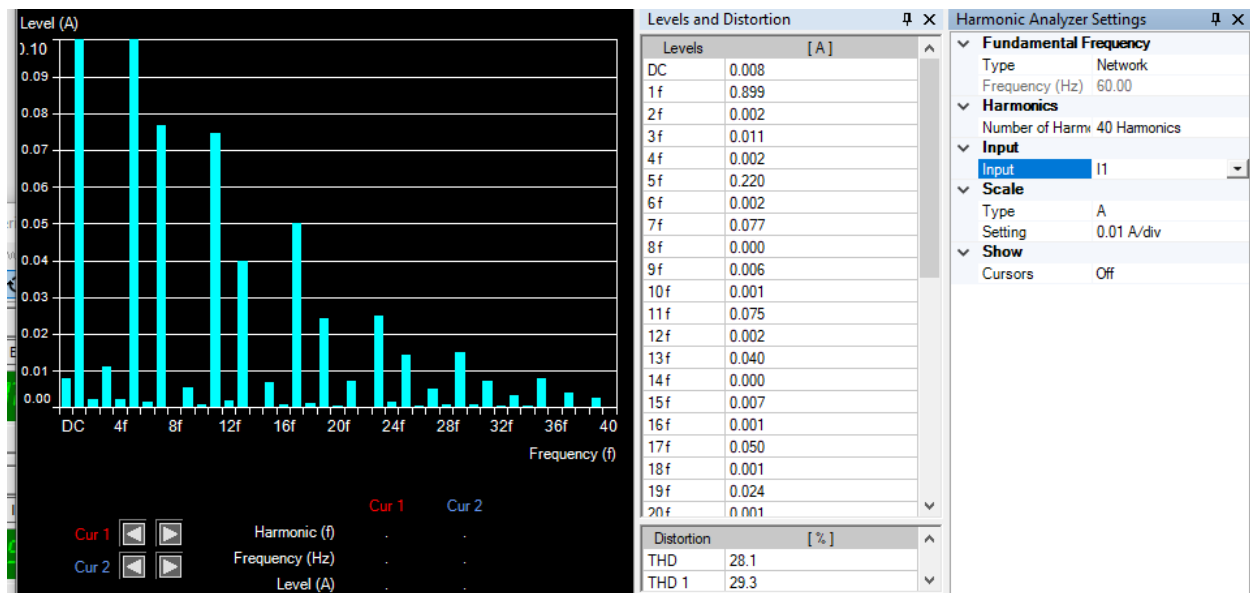


Figure 21:- The figure shows the harmonics of the input current for the DC motor – 3 phase

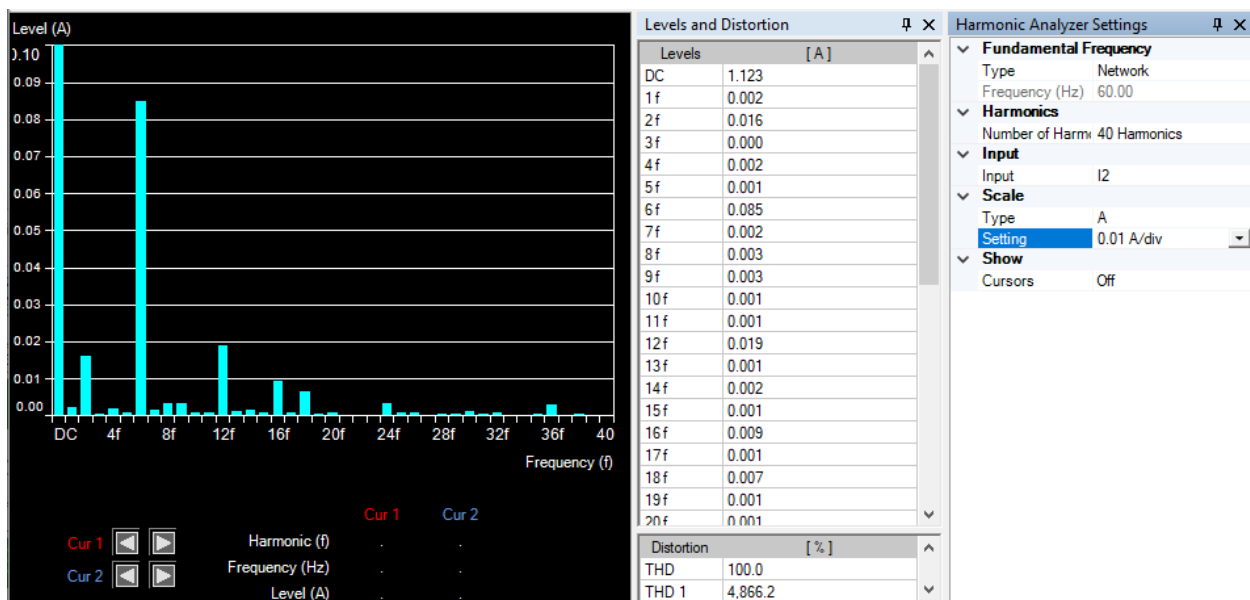


Figure 22:- The figure shows the harmonics of the output current for the DC motor – 3 phase



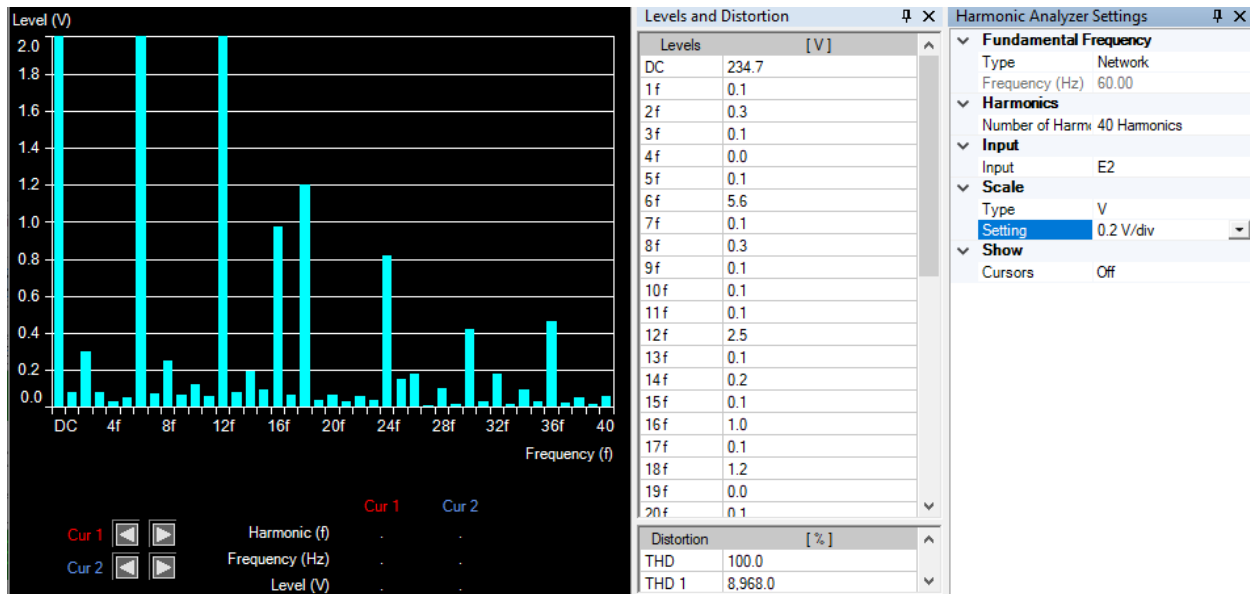


Figure 23:- The figure shows the harmonics of the output voltage for the DC motor – 3 phase

## 4 Calculations and Questions

### 4.1 Input Power Calculations

The power factor can be obtained according to following equations:

$$S = P + jQ$$

$$|S| = \sqrt{P^2 + Q^2}$$

$$\text{PowerFactor}(pf) = \cos \theta = \frac{P}{|S|}$$

Rectifier type	Load type	P (W)	Q (Var)	S (VA)	Power factor
1 phase	200 $\Omega$	17.32	-0.044	17.32	1
	Dc motor	100.6	47.72	111.34	0.9035
3 phase	200 $\Omega$	28.35×3=85.05	3.287×3=9.861	85.62	0.9933
	Dc motor	94.64×3=283.92	9.504×3=28.512	285.35	0.995

Table 1:- The table shows the calculations for the input power factor

## 4.2 Efficiency Calculations

Efficiency can be calculated as follow:

$$\eta = \frac{P_{dc}}{P_{in}}$$

Rectifier type	Load type	P <sub>dc</sub> (W)	P <sub>in</sub> (W)	$\eta$
1 phase	200 $\Omega$	16.10	17.32	0.9295
	Dc motor	96.36	100.6	0.9578
3 phase	200 $\Omega$	78.32	28.35 $\times$ 3=85.05	0.9208
	Dc motor	272.2	94.64 $\times$ 3=283.92	0.9587

Table 2:- The table shows the calculations for the efficiency

## 4.3 Efficiency Comparison

It is obvious that the power of 3-phase system is more than that of the single phase rectifier. Therefore, as we can see on Table 2, the efficiency was more in 3-phase than in the single phase. In addition, the ripple factor according to the harmonic spectrums was less in the 3-phase. We would also like to take into account that there can some errors due to our equipment used in the experiment. Finally, comparing the 200 ohm resistive load and the DC motor load; we can see from Table 2 above that, the DC motor load had more efficiency than the resistive load.

## 4.4 Power Losses Calculations

Power loss can be obtained from following equation:

$$P_{loss} = P_{in} - P_{dc}$$

Rectifier type	Load type	$P_{dc}$ (W)	$P_{in}$ (W)	$P_{loss}$ (W)
<b>1 phase</b>	200 $\Omega$	16.10	17.32	1.22
	Dc motor	96.36	100.6	4.24
<b>3 phase</b>	200 $\Omega$	78.32	$28.35 \times 3 = 85.05$	6.73
	Dc motor	272.2	$94.64 \times 3 = 283.92$	11.72

*Table 3:– The table shows the calculations of the Power Losses*

## 5 Conclusions

From the results for the single phase and the 3 phase full-wave rectifiers, we can see that the input voltage and the load type have different impacts on the efficiency. As seen on Table 2 above we can conclude that; by changing the resistive load to the DC motor load and increasing the input voltage, there will be a rise in the efficiency. This conclusion is effective on both the single phase and the 3 phase system. In addition, according to harmonics spectrum and the Y-YG connection of the transformer, we experienced less harmonics in the 3-phase as compared to the single phase for both loads; this made the waveform of the output voltage and current to have less ripples. Furthermore, the power losses are more in the DC motor as compared to that of the resistive load; this is because the DC motor has an inductive load.