

ECE4643: Power Electronics

Assignment 3: Solution

Q1:

- 1.
- 2.
- 3.
- 4.
- 5.

Q2

A DC Buck converter has an input voltage of 50 V, and an output voltage of 25 V at a switching frequency of 100 kHz. If the load is 125 W, determine:

- a) The duty cycle D .

The value of D can be determined using V_s and V_O as:

$$V_O = DV_s \implies D = \frac{V_O}{V_s} = \frac{25}{50} = 0.5$$

- b) The value of the ripple current in the inductor.

The value of the ripple current in the inductor Δi_L can be determined using the peak value of of the inductor current $I_1 = 6.25$ A and the average value of the load current I_O as:

$$I_1 = I_O + \frac{\Delta i_L}{2} \implies \Delta i_L = 2(I_1 - I_O)$$

The average value of the load current I_O can be determined from V_O and the load power P_L as:

$$P_L = V_O I_O \implies I_O = \frac{P_L}{V_O} = \frac{125}{25} = 5 \text{ A}$$

The value of Δi_L can be obtained as:

$$\Delta i_L = 2(6.25 - 5) = 2.5 \text{ A}$$

c) The value of L to limit the peak inductor current to 6.25 A.

The value of the inductor L to limit the peak inductor current to 6.25 A, i.e. $I_1 = 6.25 \text{ A}$ can be determined using Δi_L as:

$$\Delta i_L = \frac{DV_S(1-D)T}{L} \implies L = \frac{DV_S(1-D)}{f\Delta i_L} = \frac{0.5 \times 50(1-0.5)}{100 \times 10^3 \times 2.5} = 50 \mu H$$

d) The value of C to limit the output voltage ripple to 0.5%.

The value of the capacitor C to limit the voltage ripple to 0.5%, i.e. $\Delta v_O = 0.005$ can be determined as:

$$\Delta v_O = \frac{(1-D)V_O}{8LCf^2} \implies C = \frac{(1-D)V_O}{8L\Delta v_O f^2} = \frac{(1-0.5) \times 25}{8 \times 50 \times 10^{-6} \times 0.005 \times (100 \times 10^3)^2} = 625 \mu F$$

Q3:

A DC boost converter has a supply voltage of 5 V, and an output voltage of 15 V to feed a load with 25 W. If the switching frequency is 300 kHz, determine:

a) The value of L that limit the minimum inductor current to 50% of the average current.

The average value of the load current I_O can be determined from V_O and the load power

P_L as:

$$P_L = V_O I_O \implies I_O = \frac{P_L}{V_O} = \frac{25}{15} = 1.6667 \text{ A}$$

The minimum inductor current $I_2 = 0.5I_O$, where:

$$I_2 = 0.5I_O = I_O - \frac{\Delta i_L}{2} \implies \Delta i_L = 2 \times 0.5I_O = 2 \times 0.5 \times 1.6667 = 1.6667 \text{ A}$$

The value of the inductor L can be determined using Δi_L as:

$$\Delta i_L = \frac{DV_S}{fL} \implies L = \frac{DV_S}{f\Delta i_L}$$

The value of the duty cycle D can be determined using V_O and V_s as:

$$\frac{V_O}{V_s} = \frac{1}{1-D} \implies \frac{15}{5} = \frac{1}{1-D} \implies 1-D = \frac{1}{3} \implies D = \frac{2}{3} = 0.6667$$

The value of the inductor L can be evaluated as:

$$L = \frac{DV_S}{f\Delta i_L} = \frac{0.6667 \times 5}{300 \times 10^3 \times 1.66667} = 6.667 \mu\text{H}$$

b) The duty cycle D .

The value of the duty cycle D can be determined using V_O and V_s as:

$$\frac{V_O}{V_s} = \frac{1}{1-D} \implies \frac{15}{5} = \frac{1}{1-D} \implies 1-D = \frac{1}{3} \implies D = \frac{2}{3} = 0.6667$$

c) The minimum values of L and C to ensure the converter is in the continuous mode.

The minimum value of the inductor L_B can be determined as:

$$L_B = \frac{D(1-D)^2 R_L}{2f}; \quad R_L = \frac{V_O^2}{P_L} = \frac{15^2}{25} = 9 \quad \Omega$$

$$L_B = \frac{0.6667 \times (1 - 0.6667)^2 \times 9}{2 \times 300 \times 10^3} = 1.11 \quad \mu H$$

The minimum value of the capacitor C_B can be determined as:

$$C_B = \frac{D}{2fR_L} = \frac{0.6667}{2 \times 300 \times 10^3 \times 9} = 0.13 \quad \mu F$$

- d) The value of current ripple in the inductor, and the value of the voltage ripple in the capacitor.

The value of Δi_L was determined as:

$$\Delta i_L = 2 \times 0.5 I_O = 2 \times 0.5 \times 1.6667 = 1.6667 A$$

The value of Δv_O can be determined as:

$$\Delta v_O = \Delta v_C = \frac{I_O D}{fC} = \frac{1.66667 \times 0.66667}{300 \times 10^3 \times 10 \times C_B}$$

Please note that since the converter is in the continuous mode ($L > L_B$), then

let $C = 10C_B = 1.3 \mu F$.

$$\Delta v_O = \Delta v_C = \frac{1.66667 \times 0.66667}{300 \times 10^3 \times 1.3 \times 10^{-6}} = 2.85 \quad V$$

Q4

Design a buck DC converter to supply a load with 3.0 kW at 150 V from a 250 V supply. The desired DC PEC is to operate in the continuous conduction mode, and has to maintain the ripple in the inductor current as $\Delta i_L \leq 0.5$ A. Specify the values of D , L , C , and switching frequency.

The duty cycle D can be determined using V_O and V_s as:

$$\frac{V_O}{V_s} = D \Rightarrow \frac{150}{250} = 0.6$$

The average value of the load current I_O can be determined using V_O and P_L as:

$$I_O = \frac{P_L}{V_O} = \frac{3000}{150} = 20 \text{ A}$$

The value of the inductance L can be determined using the ripple in the inductor current Δi_L as:

$$\Delta i_L = \frac{DV_s(1-D)T}{L} \Rightarrow L = \frac{DV_s(1-D)}{f_s \Delta i_L}$$

Let the switching frequency be set at $f_s = 15$ kHz. The selection of f_s leads to:

$$L = \frac{0.6 \times 250 \times (1 - 0.6)}{15 \times 10^3 \times 0.5} = 8.0 \text{ mH}$$

The value of C requires determining L_B , as:

$$L_B = \frac{R_L(1-D)}{2f_s}$$

The value of R_L can be obtained as:

$$R_L = \frac{V_O}{I_O} = \frac{150}{20} = 7.5 \Omega$$

$$L_B = \frac{7.5 \times (1 - 0.6)}{2 \times 15 \times 10^3} = 0.1 \text{ mH}$$

The value of C_B can be determined as:

$$C_B = \frac{1 - D}{16L_B f_s^2} = \frac{1 - 0.6}{16 \times 0.1 \times 10^{-3} \times (15 \times 10^3)^2} = 1.11 \mu F$$

In order to ensure CCM, let $C = 5 \times C_B = 5 \times 1.11 \times 10^{-6} = 5.56 \mu F$

The MATLAB/SIMULINK File Q4-A3.slx has a model for the designed buck dc PEC.