

EE4643: Power Electronics

Assignment 1: Solutions

Q1:

Q2 Consider the converter shown in Figure 1. Assume that the MOSFET Q and diode D are ideal in that their ON-state voltages are zero, and they can turn turn-ON and turn-OFF instantly. The waveform of the diode switching is also included in Figure 1.

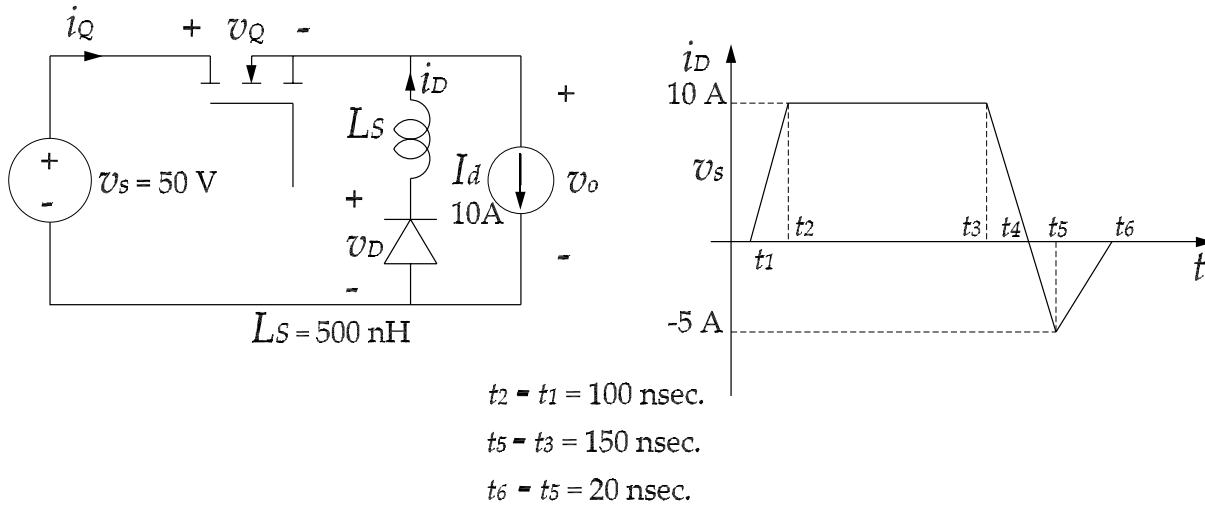


Figure 1: The converter for Q2.

1. Calculate and sketch to scale the diode and MOSFET voltages v_D and v_Q , and i_Q ;

The waveforms of i_D , v_D , v_Q , and i_Q are shown in Figure 2.

2. Estimate the switching losses in the diode and the MOSFET if the converter is operated at a switching frequency of $f_s = 200\text{ kHz}$.

The switching losses will be determined for ON and OFF switching for both D and Q .

(a) **D:** The instantaneous ON switching losses $(P_{ON1})_D$ are determined as:

$$(P_{ON1})_D = v_D(t)i_D(t); \quad v_D(t) = v_s \left(1 - \frac{t}{t_2}\right); \quad i_D(t) = \frac{I_d}{t_2}t$$

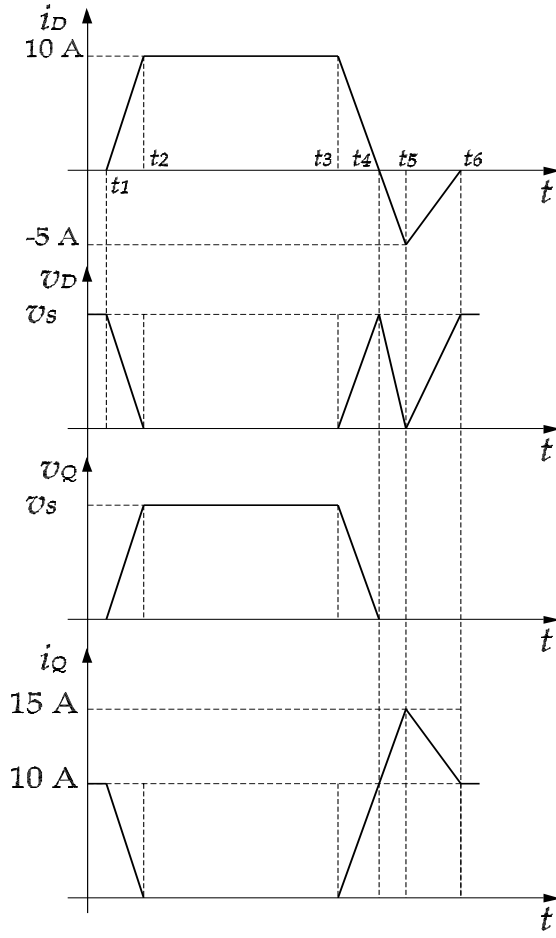


Figure 2: The waveforms of i_D , v_D , v_G , and i_G .

$$(P_{ON1})_D = \frac{v_s I_d}{t_2} t - \frac{v_s I_d}{t_2^2} t^2$$

The energy losses during ON switching $(W_{ON})_D$ is determined as:

$$(W_{ON})_D = \int_0^{t_2} (P_{ON1})_D dt = \int_0^{t_2} \frac{v_s I_d}{t_2} t dt - \int_0^{t_2} \frac{v_s I_d}{t_2^2} t^2 dt = \frac{v_s I_d}{2} t_2 - \frac{v_s I_d}{3} t_2$$

The average power losses during ON switching $(P_{ON})_D$ is determined as:

$$(P_{ON})_D = (W_{ON})_D \times f_s = 1.6667 \text{ W}$$

The instantaneous OFF switching power losses $(P_{OFF1})_D$ are determined as:

$$(P_{OFF1})_D = v_D(t)i_D(t);$$

During the OFF switching $i_D(t)$ has 2 portions, which can be expressed as:

$$(i_D(t))_1 = I_d - \frac{I_d + 5}{t_5}t, \quad (i_D(t))_2 = \frac{5}{t_6}t - 5$$

$v_D(t)$ has 3 portions that can be expressed as:

$$(v_D(t))_1 = \frac{v_s}{t_4}t, \quad (v_D(t))_2 = v_s \left(1 - \frac{1}{t_5}t\right), \quad (v_D(t))_3 = \frac{v_s}{t_6}t$$

The energy losses during OFF switching $(W_{OFF})_D$ is determined as:

$$\begin{aligned} (W_{OFF})_D &= \int_{t_3}^{t_4} (v_D(t))_1 (i_D(t))_1 dt + \int_{t_4}^{t_5} (v_D(t))_2 (i_D(t))_1 dt + \int_{t_5}^{t_6} (v_D(t))_3 (i_D(t))_2 dt \\ (W_{OFF})_D &= \int_0^{t_4-t_3} (v_D(t))_1 (i_D(t))_1 dt + \int_0^{t_5-t_4} (v_D(t))_2 (i_D(t))_1 dt + \int_0^{t_6-t_5} (v_D(t))_3 (i_D(t))_2 dt \\ (W_{OFF})_D &= \frac{I_d v_s}{2t_4} (t_4 - t_3) - \left(\frac{I_d v_s + 5v_s}{3t_4 t_5} \right) (t_4 - t_3)^3 + v_s I_d (t_5 - t_4) - \left(\frac{I_d v_s + 5v_s}{2t_5} \right) (t_5 - t_4)^2 \\ &\quad - \frac{I_d v_s}{2t_5} (t_5 - t_4)^2 + \left(\frac{I_d v_s + 5v_s}{3t_5^2} \right) (t_5 - t_4)^3 + \frac{5v_s}{3t_6^2} (t_6 - t_5)^3 - \frac{5v_s}{2t_6} (t_6 - t_5)^2 \\ (W_{OFF})_D &= 2.1307 \times 10^{-5} \text{ J} \end{aligned}$$

Assuming that t_4 is the mid point between t_3 and t_5 , the average power losses during OFF switching $(P_{OFF})_D$ is determined as:

$$(P_{OFF})_D = (W_{OFF})_D \times f_s = 4.2614 \text{ W}$$

The switching power losses for D are $(P_{SW})_D$ is determined as:

$$(P_{SW})_D = (P_{ON})_D + (P_{OFF})_D = 5.9281 \text{ W}$$

(b) **Q:**

The instantaneous OFF switching losses $(P_{OFF1})_Q$ are determined as:

$$(P_{OFF1})_Q = v_Q(t)i_Q(t); \quad v_Q(t) = \frac{v_s}{t_2}t; \quad i_Q(t) = I_d \left(1 - \frac{t}{t_2}\right)$$

$$(P_{OFF1})_Q = \frac{v_s I_d}{t_2}t - \frac{v_s I_d}{t_2^2}t^2$$

The energy losses during OFF switching $(W_{OFF})_Q$ is determined as:

$$(W_{OFF})_Q = \int_0^{t_2} (P_{ON1})_Q dt = \int_0^{t_2} \frac{v_s I_d}{t_2} t dt - \int_0^{t_2} \frac{v_s I_d}{t_2^2} t^2 dt = \frac{v_s I_d}{2} t_2 - \frac{v_s I_d}{3} t_2$$

The average power losses during OFF switching $(P_{OFF})_Q$ is determined as:

$$(P_{OFF})_Q = (W_{OFF})_Q \times f_s = 1.6667 \text{ W}$$

The instantaneous ON switching power losses $(P_{ON1})_Q$ are determined as:

$$(P_{ON1})_Q = v_Q(t)i_Q(t);$$

$$i_Q(t) = \frac{I_d + 5}{t_5}t, \quad v_Q(t) = v_s \left(1 - \frac{t}{t_4}\right)$$

The value of $(P_{ON1})_Q$ is determined as:

$$(P_{ON1})_Q = \frac{15v_s}{t_5}t - \frac{15v_s}{t_4 t_5}t^2$$

The energy losses during ON switching $(W_{ON})_Q$ is determined as:

$$(W_{ON})_Q = \int_0^{t_4} (P_{ON1})_Q dt = \int_0^{t_4} \frac{15v_s}{t_5} t dt - \int_0^{t_4} \frac{15v_s}{t_4 t_5} t^2 dt = \frac{15v_s}{2t_5} t_4^2 - \frac{15v_s}{3t_5} t_4^2$$

Assuming that t_4 is the mid point between t_3 and t_5 , the average power losses during ON switching $(P_{ON})_Q$ is determined as:

$$(P_{ON})_Q = (W_{ON})_Q \times f_s = 0.9375 \text{ W}$$

The switching power losses for Q are $(P_{SW})_Q$ are determined as:

$$(P_{SW})_Q = (P_{ON})_Q + (P_{OFF})_Q = 2.61 \text{ W}$$

3. If the total losses for the MOSFET and diode are modeled as:

$$P_{LQ} = 20 + 50 \times 10^{-6} f_s \text{ and } P_{LD} = 10 + 0.44 \times 10^{-6} f_s$$

where f_s is the switching frequency. Determine the maximum switching frequency so that the junction temperature of both Q and D does not exceed 120°C . Assume that both D and Q are mounted on the same heat sink, and the ambient temperature is 40°C . The thermal resistances are in $^\circ\text{C}/\text{W}$ as:

$$(R_{\theta JC})_Q = 0.8, (R_{\theta CS})_Q = 1.2,$$

$$(R_{\theta JC})_D = 0.6, (R_{\theta CS})_D = 1.4,$$

$$R_{\theta SA} = 0.4$$

The equivalent thermal circuit for D , Q , cases, and the heat sinks are shown in Figure 3.

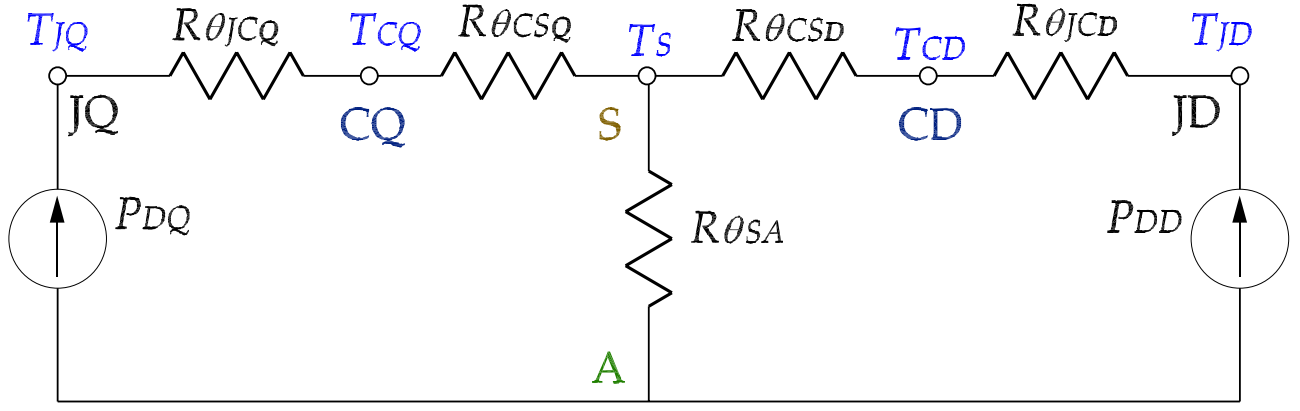


Figure 3: The thermal circuit for the Q2-3.

$$T_{JQ} - T_S = P_{LQ} \left((R_{\theta JC})_Q + (R_{\theta CS})_Q \right) \Rightarrow T_S = 120 - 2P_{LQ}$$

$$T_S - T_A = (P_{LQ} + P_{LD}) R_{\theta SA} \Rightarrow 120 - 2P_{LQ} - 40 = (30 + 50.44 \times 10^{-6} f_s) 0.4$$

$$80 - 40 - 100 \times 10^{-6} f_s = 12 + 20.176 \times 10^{-6} f_s \Rightarrow f_s = 232.997 \text{ kHz}$$

Q3: Design a BJT drive circuit with an initial base current of 5 A, for this BJT having $I_C = 25 \text{ A}$. This BJT is to be switched at a switching frequency $f_s = 8 \text{ kHz}$ with a duty cycle of 75%. This BJT has $h_{fe} = 30$, a drive signal is 10 V (ON), and $V_{BE}(\text{sat}) = 1 \text{ V}$.

The schematics of the driver is shown in Figure 4.

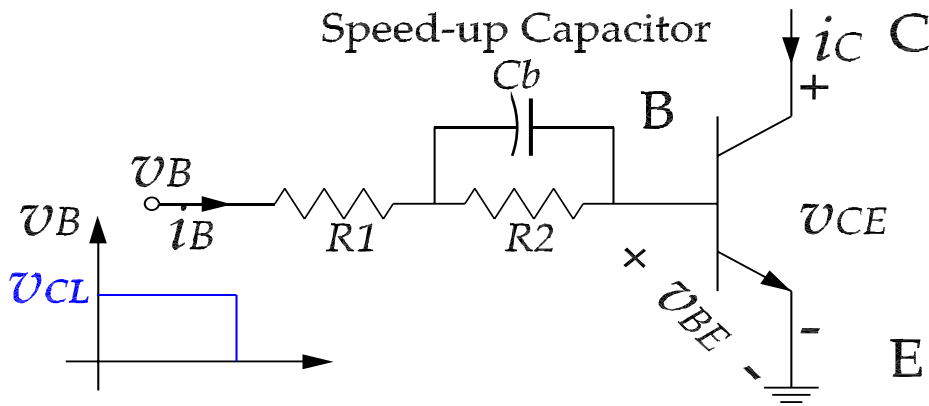


Figure 4: The desired drive circuit for the BJT

The initial base activation current $I_{B1} = 5$. The minimum current to ensure an ON state is I_{B2} that can be determined as:

$$I_{B2} = \frac{I_C}{h_{fe}} = \frac{25}{30} = 0.8333 \text{ A}$$

Assume overdrive required current I_{B2} as:

$$I_{B2} = 3 \times I_{B2} = 2.5 \text{ A}$$

$$I_{B1} = \frac{V_B - V_{BE}(sat)}{R_1} = \frac{10 - 1}{R_1} \Rightarrow R_1 = \frac{9}{5} = 1.8 \text{ } \Omega$$

$$I_{B2} = \frac{V_B - V_{BE}(sat)}{R_1 + R_2} \Rightarrow R_2 = \frac{9}{2.5} - 1.8 = 1.8 \text{ } \Omega$$

Assume charging time (5τ) to be $0.2T_{ON}$, the value of T_{ON} can be determined as:

$$D = \frac{T_{ON}}{T_s} = T_{ON} \times f_s \Rightarrow T_{ON} = \frac{0.75}{8000} = 93.75 \text{ } \mu sec.$$

$$5\tau = 0.2 \times 93.75 \times 10^{-6} = 18.75 \times 10^{-6} \Rightarrow \tau = 3.75 \times 10^{-6} \text{ } sec$$

The value of C is determined as:

$$\tau = R_{eq}C; R_{eq} = R_1 // R_2 = 0.9 \text{ } \Omega$$

get the value of $C = 4.2 \mu F$.