



CALCULATION SHEET

Sheet: 7 of 7

| | | | | | |
|-----------------------------|-------|----------------|------|---------|-------|
| TITLE: Power Electronics | SITE: | DATE: | REV. | DONE BY | APPR. |
| DESCRIPTION: Theoretical | | April 14, 2015 | | | |
| PROJECT ID: | | | | | |
| REFERENCE(S): | | | | | |

Explain Selective Harmonic Elimination with Graphs.. (SHE)

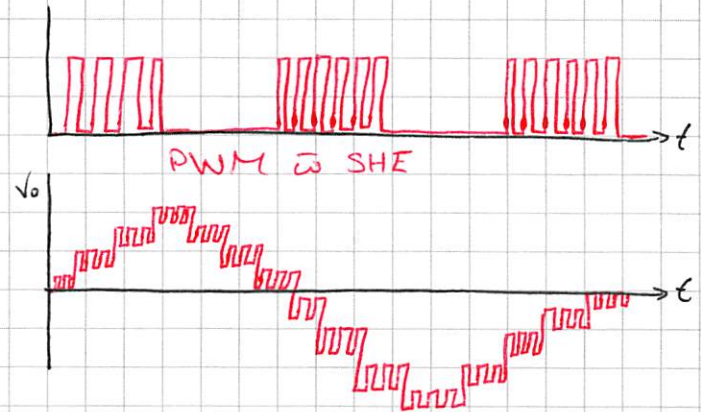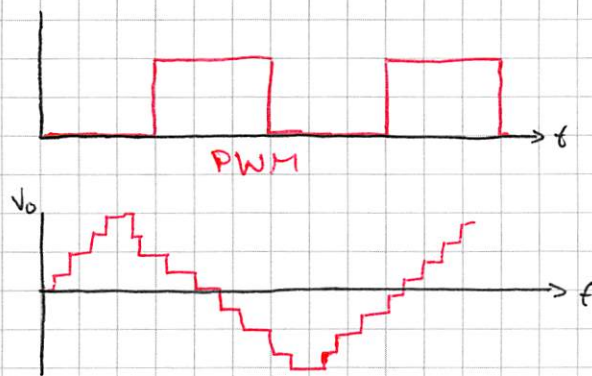- Selective Harmonic Elimination (SHE) introduces additional notches in the basic voltage waveform of the square-wave inverter.
- The output voltage is "chopped" a number of times at an angle to eliminate selected harmonic components



Functional Considerations for 3 ϕ Inverters

- Need good snubber circuits to reduce voltage spikes between switching
- The switching element activation should ensure 120° phase separation between outputs
- Must keep quarter-wave symmetry
- Switching Time
- Provide Voltage & Frequency Control
- Must use complimentary branch switching as to not short circuit the supply
↳ Blanking time
- Filtering
- Modulation Technique to eliminate harmonics & improve fundamental

List 3 different methods for eliminating or reducing output harmonics in inverters.

- Low Pass Filter on output
- Selective Harmonic Elimination
- Multiple PWM
- Harmonic Injection PWM
- Non-sinusoidal Modulation
- Staircase PWM
- Trapezoidal PWM
- Random PWM
- Space Vector Modulation
- Hysteresis-band Current Control (HBCC)

Considerations for selecting m_f

- Always has to be an odd integer to create blanking time
- Higher values of m_f result in higher/increased switching losses
- Higher values of m_f also result in lower efficiency.

| CALCULATION SHEET | | | | Sheet: 6 of 7 | |
|---|-------|----------------|------|---------------|-------|
| TITLE: Power Electronics | SITE: | DATE: | REV. | DONE BY | APPR. |
| DESCRIPTION: Theoretical | | April 14, 2015 | | | |
| PROJECT ID: | | | | | |
| REFERENCE(S): | | | | | |
| <p>What is the major challenge for operating an inverter?</p> <ul style="list-style-type: none"> - Whenever the voltage $V_o(t)$ and current $i_o(t)$ are not the same polarity, then $i_o(t)$ flows through the anti-parallel diodes, otherwise, it flows through the switching elements - Limited Fundamental Component at the output - Harmonics - THD must meet grid requirements, if being grid-connected - Maintain periodic output to prevent DC in load, make sure to have quarter-wave symmetry <p>What is blanking time and why is it important?</p> <ul style="list-style-type: none"> - Blanking time is the delay between switching pulses (ON-OFF-ON) - Important so two switching elements in the same leg are not on at the same time which would short the DC input supply. - Finite switching time delay to ensure no short circuit across DC input <p>Briefly explain the basic concept of PWM technique for 1Ø inverters.</p> <ul style="list-style-type: none"> - Allows elimination of specific harmonic components - Output voltage & current control - Sine wave (reference) compared with Triangular/Sawtooth waveforms - Can be half or full-bridge - V_s has a pulse when Q_1 & Q_2 or Q_3 & Q_4 are activated, allowing i_o to flow - Adjust δ width to remove harmonic, width of pulses has to be determined off line <p>Output filters in inverters suffer from a main functional limitation, what is this limitation?</p> <ul style="list-style-type: none"> - Low Pass filters designed for cutoff frequency (Size of components will depend on switching freq, technique and # of phases) - Cannot help the fundamental component/value (ie. can't boost the fundamental) <ul style="list-style-type: none"> ↳ Eliminates harmonics for a Better THD but... ↳ Energy in the fundamental remains the same and the energy in the harmonics is lost | | | | | |

CALCULATION SHEET

Sheet: 5 of 7

TITLE: Power Electronics

SITE:

DATE:

REV.

DONE BY

APPR.

DESCRIPTION:

Theoretical

April 14, 2015


PROJECT ID:

REFERENCE(S):

List 2 differences between the flyback and buck-boost DC-DC PECs.

- Flyback converters are isolated, where Buck-Boost converters are not.
- Flyback converters can supply multiple loads by using a multi-tap, high freq. transformer, where Buck-Boost PECs can only supply 1 load/branch
- Buck-Boost PECs can handle much higher powers than Flyback converters.

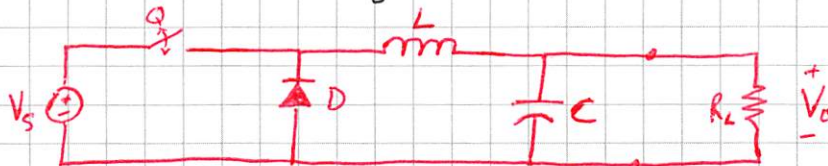Draw the circuit Diagram for the Buck DC-DC PEC.



Draw the circuit Diagram for the Boost DC-DC PEC.



Draw the circuit Diagram for the Buck-Boost PEC.



*Note inverted output.

What is the main concept of operating DC-AC converters?

- DC-AC converters have a main function of converting DC voltages/currents into 1Ø or 3Ø AC voltages & currents, along with providing voltage & frequency control with only one power stage. This function is achieved by operating inverter switching elements in a periodic sequential manner of either fully ON or fully OFF
- Periodic & Sequential Switching, with complementary switching actions

List 3 different methods for eliminating or reducing the output harmonics in inverter

- Low pass filter on output
- Multiple pulse width Modulation
- SHE (Selective Harmonic Elimination) ~ multiple notches remove/eliminate harmonics
- Topology of the inverter

| CALCULATION SHEET | | | | Sheet: 4 of 7 | |
|---|----------------|-------|------|---------------|-------|
| TITLE: Power Electronics | SITE: | DATE: | REV. | DONE BY | APPR. |
| DESCRIPTION: Theoretical | April 14, 2015 | | | | |
| PROJECT ID: | | | | | |
| REFERENCE(S): | | | | | |
| <p>The analysis of DC switch mode converters makes assumptions of periodic steady-state assumptions operation of these converters, what are the implications of such assumptions?</p> <ul style="list-style-type: none"> - The average voltage across the inductor is zero - The average current through the capacitor is zero - These assumptions facilitate/allow for a simplified analysis - The assumptions also ignore the parasitics of capacitors, treating them as ideal elements, further allowing for simplified analysis. <p>Why is it recommended to operate Buck Converters with high values of Duty Cycle ($D \rightarrow 1$)?</p> <ul style="list-style-type: none"> - In a Buck converter, higher output current, I_o, is desired, so we need a longer 'ON' time, and thus, higher inductor current <li style="padding-left: 20px;">$I_o \uparrow = V_o \downarrow$ Duty cycle is similar to the turns Ratio in a transformer - Continuous mode <p>Why is it recommended to operate Boost converters with low values of duty cycle ($D \rightarrow 0$)?</p> <ul style="list-style-type: none"> - In a boost converter, less 'ON' time results in more capacitor charging $\rightarrow V_o \uparrow$ - Converter become unstable/non-linear at higher Duty Cycles ($D > 0.8$) - Fairly linear relationship at low values of Duty Cycle - At duty cycles of 0.9999 (≈ 1), switch is always ON, inductor saturates & becomes a current source, Diode is always reverse biased <li style="padding-left: 20px;">\rightarrow No current goes to the load, any voltage can be seen at output (random) but no current $I_o \approx 0$ <p>Describe the function of a Buck-Boost Converter.</p> <p>A Buck-Boost converter can increase & decrease the output voltage</p> <ul style="list-style-type: none"> - $D > 0.5 \rightarrow$ Acts as a Boost converter & $V_o > V_s$ - $D < 0.5 \rightarrow$ Acts as a Buck converter & $V_o < V_s$ <p>This converter inverts the output voltage compared to Buck or Boost converters.</p> <p>The DC Flyback converter can be switched at higher frequencies than switch mode DC converters, what supports such a feature?</p> <ul style="list-style-type: none"> - The DC Flyback converter has a high frequency transformer which isolates the output from the input <li style="padding-left: 20px;">\rightarrow This also serves as protection from current spikes. | | | | | |

CALCULATION SHEET

Sheet: 3 of 7

TITLE: Power Electronics

SITE:

DATE:

REV.

DONE BY

APPR.

DESCRIPTION:

Theoretical

April 14, 2015

PROJECT ID:

REFERENCE(S):

When designing input filters for AC-DC converters, what are the main trade-offs in selecting the components?

- Capacitors & Inductors improve voltage & current signals, but higher current drawn from AC sources (More power losses, heat, & lower efficiency)
- Harmonic Distortion is a concern
- Reduced THD_i (L), but brings down PF, so a capacitor is needed which will end up changing the THD_i
- Must be aware of heating effects
- Make sure they don't affect switching

What are the main differences between designing input and output LC filters for 1Ø & 3Ø full-wave rectifiers?

- When designing the input filter, in a single phase system, we are concerned about cleaning the 3rd harmonic, requires a better & more expensive filter
- When designing the input filter, in a 3Ø system, we are concerned about cleaning the 5th harmonic, a less sophisticated filter is required.
- When Designing the output filter for:
 - 1Ø system - concerned about cleaning 2nd harmonic (Difficult)
 - 3Ø system - concerned about cleaning 6th harmonic (Easier)
- It is easier to filter the higher harmonics.

List 3 objectives for designing input and output filters for AC-DC power electronic converters.

- Must Reduce THD_i to be less than 5% (by standards)
- Input filters of a 3Ø PEC (AC-DC) must target the 5th harmonic, while the input filter of a 1Ø AC-DC PEC must target the 3rd harmonic
- Output filters of a 3Ø ACDC PEC must target the 6th harmonic, while the output filter of a 1Ø ACDC PEC must target the 2nd harmonic
- In the design stage, you are seeking to get the best power factor preferably PF > 70%

What is the main concept of DC switch mode converters?

- Switching must be sequential & periodic
- Connect & Disconnect a load to the supply on a periodic basis. The duration of each connect & disconnect have to be based on a certain level of control
- Output can be adjusted by varying the duty cycle
↳ PWM controlled
- Single Phase
- Regulated

CALCULATION SHEET

Sheet: 2 of 7

| | | | | | |
|--------------------------|-------|----------------|------|---------|-------|
| TITLE: Power Electronics | SITE: | DATE: | REV. | DONE BY | APPR. |
| DESCRIPTION: Theoretical | | April 14, 2015 | | | |
| PROJECT ID: | | | | | |
| REFERENCE(S): | | | | | |

List 3 factors that can influence power losses (switching & conduction) in power electronic devices / switching elements.

- Switching Frequency
- Use of a Snubber Circuit
- Switching Times
- 'ON' voltage & current ratings
- Leakage Current
- Duty cycle (maybe)
- Device characteristics

Inductive loads can impact the specifications for heat sinks, explain why.

- In cases of inductive loads, the switching ~~elements~~ losses are higher because the current being drawn takes a longer time to change due to the inductance
- Because switching losses are higher, the sink must be designed / specified to dissipate the extra heat from the additional Power Losses.

What is the main concept of AC Rectification?

- Sequential Switching
- Periodic Patterns
- Not allowing signals to swing below zero volts
- Making AC signals DC signals

The inductance behaves in steady-state as a short circuit to DC currents & voltages, why do inductive loads represent a major operational concern in an AC-DC Converter?

- Inductive loads can cause / force the diodes to conduct while reverse biased.
↳ This will fry the diodes ↳ or switching elements
- Can be fixed with a free-wheeling Diode
- Delays input current → can fry the component

What are the main differences between the diodes used in an AC-DC rectifier and the free-wheeling diodes?

- Free-wheeling diodes have shorter switching times than the normal AC-DC diodes
- Used to eliminate sudden changes in voltage & current
↳ Part of a snubber circuit
- Conduct when other diodes are reverse biased.

What are the main requirements for operating & controlling AC-DC Thyristor based converters?

- Phase-controlled thyristors must be capable of handling high voltages & currents with low conduction losses.
- Thyristors begin conducting when given a voltage signal / pulse from a controller & stop conducting when the voltage across them goes negative.

CALCULATION SHEET

Sheet: 1 of 7

| | | | | | |
|-----------------------------|-------|----------------|------|---------|-------|
| TITLE: Power Electronics | SITE: | DATE: | REV. | DONE BY | APPR. |
| DESCRIPTION: Theoretical | | April 14, 2015 | | | |
| PROJECT ID: | | | | | |
| REFERENCE(S): | | | | | |

What are the main differences between current-controlled & voltage-controlled power Electronic switching elements?

- Driver circuits are different
- Current Driven devices require a good amount of base current to get going, this is the reason for slower switching times
- Voltage-controlled requires a voltage signal to change operating states, versus a current-controlled which requires a current signal
- Different switching times
 - Current Driven \rightarrow Slower (ie. BJT)
 - Voltage Driven \rightarrow Faster (ie. MOSFET, IGBT, Thyristor)

Power Electronic Converters are described as sequentially operated switching elements. What are the requirements for maintaining such sequential switching activities?

- Switching from ON to OFF states and back on (OFF \rightarrow ON)
- Switching Time is constant
- The sequence/pattern of ON-OFF-ON-OFF is fixed
- The switching can be used to convert voltage & current magnitudes, frequencies or polarities

When designing a heat sink for a power electronic element, what needs to be considered?

- Power Losses (conduction & switching)
- Material of Device
- Type of cooling (air, fan, gas, liquid)
- Environment of Implementation
- Thermal Resistance of Sink
- Size Constraints
- Maximum Voltage & Current
- Ambient Temperature
- Electrical Isolation

How Can a snubber circuit provide limitations on voltage & current changes in power electronic switching elements?

- The use of an inductor in a snubber circuit will limit current changes, especially at high switching frequencies because it appears as high impedance \rightarrow resists changes in current when energizing & de-energizing
- The use of a capacitor in a snubber circuit limits the voltage changes due to the charging & discharging characteristics. \rightarrow Also decreases power losses.